

Tutorial-3 Solution

1. Series combination of n-MOS is equivalent to AND and parallel combination is equivalent to OR


$$\text{So, } Y = \overline{C.(A + B)}$$

$$Y = \overline{C} + \overline{(A + B)}$$


$$Y = \overline{C} + \overline{A}.\overline{B}$$

2. XOR (X, Y)

3.

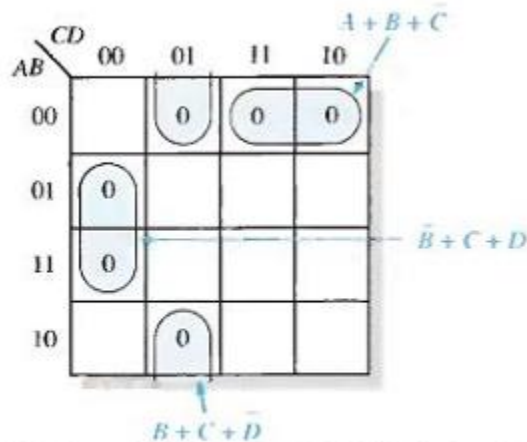

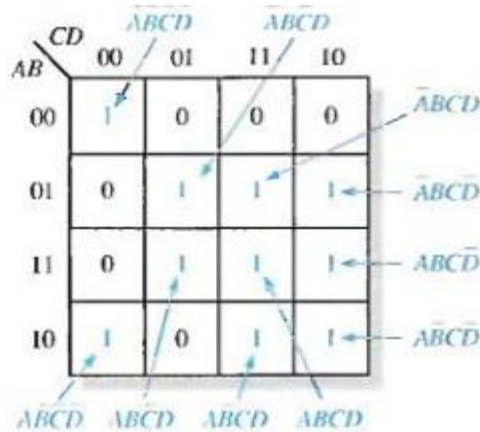
(a) Minimum POS: $(A + B + C)(\overline{B} + C + D)(B + C + \overline{D})$



(b) Standard SOP:

$$\overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + A\overline{B}C\overline{D} + A\overline{B}CD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + A\overline{B}C\overline{D} + A\overline{B}CD$$

4.

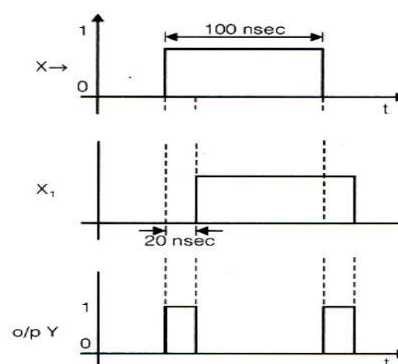

5.

X	Y	Q	Z
0	0	OFF	0
0	+5V	OFF	+5V
+5V	0	ON	0
+5V	+5V	ON	0

$$Z = \bar{X}Y$$

- 6. NOR
- 7. NOR Gate
- 8. XY
- 9. NAND

10.

		YZ			
WX		[00] Y+Z	[01] Y+Z'	[11] Y'+Z'	[10] Y'+Z
[00] W+X	0	0	1	0	
[01] W+X'	0	0	0	1	
[11] W'+X'	1	1	0	1	
[10] W'+X	1	1	1	0	

Now we will write down the marked groups and find the reduced expression.

$$\begin{aligned}
 \text{quad} &= M0 \cdot M1 \cdot M4 \cdot M5 \\
 &= [(W+X+Y+Z) \cdot (W+X+Y+Z')] \\
 &\cdot [(W+X'+Y+Z) \cdot (W+X'+Y+Z')] \\
 &= (W+X+Y) \cdot (W+X'+Y) \quad [Z' \text{ changed, so removed}] \\
 &= (W+Y) \quad [X' \text{ changed, so removed}]
 \end{aligned}$$

$$\begin{aligned}
 \text{1st pair} &= M7 \cdot M15 \\
 &= [(W+X'+Y'+Z') \cdot (W'+X'+Y'+Z')] \\
 &= (X'+Y'+Z') \quad [W' \text{ changed to } W, \text{ so removed}]
 \end{aligned}$$

$$\begin{aligned}
 \text{2nd pair} &= M2 \cdot M10 \\
 &= [(W+X+Y'+Z) \cdot (W'+X+Y'+Z)] \\
 &= (X+Y'+Z) \quad [W' \text{ changed to } W, \text{ so removed}]
 \end{aligned}$$

Now we AND (.) the results to get the final reduced expression.

$$F = (W+Y) \cdot (X'+Y'+Z') \cdot (X+Y'+Z)$$