



Boolean Algebra



LOGIC GATES

Formal logic: In formal logic, a statement (proposition) is a declarative sentence that is either true(1) or false (0).

It is easier to communicate with computers using formal logic.

- **Boolean variable:** Takes only two values – either true (1) or false (0).

They are used as basic units of formal logic.



Boolean function and logic diagram

- **Boolean function:** Mapping from Boolean variables to a Boolean value.
- **Truth table:**
 - Represents relationship between a Boolean function and its binary variables.
 - It enumerates all possible combinations of arguments and the corresponding function values.






Boolean function and logic diagram

- **Boolean algebra:** Deals with binary variables and logic operations operating on those variables.
- **Logic diagram:** Composed of graphic symbols for logic gates. A simple circuit sketch that represents inputs and outputs of Boolean functions.




Gates

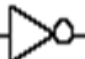- Refer to the hardware to implement Boolean operators.
- The most basic gates are

Name	Graphic symbol	Algebraic function	Truth table															
Inverter	A  x	$x = A'$	<table> <tr> <th>A</th> <th>x</th> </tr> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </table>	A	x	0	1	1	0									
A	x																	
0	1																	
1	0																	
AND	A  B x	$x = AB$	<table> <tr> <th>A</th> <th>B</th> <th>x</th> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </table> <p>True if both are true.</p>	A	B	x	0	0	0	0	1	0	1	0	0	1	1	1
A	B	x																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR	A  B x	$x = A + B$	<table> <tr> <th>A</th> <th>B</th> <th>x</th> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </table> <p>True if either one is true.</p>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	1
A	B	x																
0	0	0																
0	1	1																
1	0	1																
1	1	1																

Boolean function and truth table

- Other common gates include:

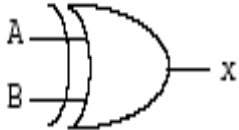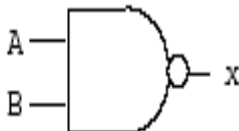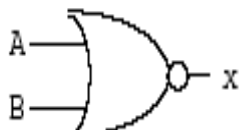Name	Graphic symbol	Algebraic function	Truth table															
Exclusive-OR (XOR)		$x = A \oplus B$ $= A'B + AB'$	<table><tr><th>A</th><th>B</th><th>x</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	0
A	B	x																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
NAND		$x = (AB)'$	<table><tr><th>A</th><th>B</th><th>x</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	x	0	0	1	0	1	1	1	0	1	1	1	0
A	B	x																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$x = A + B$	<table><tr><th>A</th><th>B</th><th>x</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	x	0	0	1	0	1	0	1	0	0	1	1	0
A	B	x																
0	0	1																
0	1	0																
1	0	0																
1	1	0																

Parity check: True if only one is true.

Inversion of AND.

Inversion of OR.



BASIC IDENTITIES OF BOOLEAN ALGEBRA

- ***Postulate 1 (Definition)***: A Boolean algebra is a closed algebraic system containing a set K of two or more elements and the two operators \cdot and $+$ which refer to logical AND and logical OR



Basic Identities of Boolean Algebra (Existence of 1 and 0 element)

$$(1) x + 0 = x$$

$$(2) x \cdot 0 = 0$$

$$(3) x + 1 = 1$$

$$(4) x \cdot 1 = x$$

(Table 1-1)



Basic Identities of Boolean Algebra (Existence of complement)

$$(5) \ x + x = x$$

$$(6) \ x \cdot x = x$$

$$(7) \ x + x' = x$$

$$(8) \ x \cdot x' = 0$$



Basic Identities of Boolean Algebra (Commutativity):

$$(9) \ x + y = y + x$$

$$(10) \ xy = yx$$



Basic Identities of Boolean Algebra (Associativity):

$$(11) \ x + (y + z) = (x + y) + z$$

$$(12) \ x (yz) = (xy) z$$



Basic Identities of Boolean Algebra (Distributivity):

$$(13) \ x (y + z) = xy + xz$$

$$(14) \ x + yz = (x + y)(x + z)$$



Basic Identities of Boolean Algebra (DeMorgan's Theorem)

$$(15) \quad (x + y)' = x' y'$$

$$(16) \quad (xy)' = x' + y'$$



Basic Identities of Boolean Algebra (Involution)

$$(17) (x')' = x$$

Function Minimization using Boolean Algebra

■ *Examples:*

$$(a) \ a + ab = a(1+b)=a$$

$$(b) \ a(a + b) = a.a + ab = a + ab = a(1+b) = a.$$

$$(c) \ a + a'b = (a + a')(a + b) = 1(a + b) = a + b$$

$$(d) \ a(a' + b) = a.a' + ab = 0 + ab = ab$$



Try

- $F = abc + abc' + a'c$



The other type of question

Show that;

$$1- ab + ab' = a$$

$$2- (a + b)(a + b') = a$$

$$1- ab + ab' = a(b+b') = a.1=a$$

$$\begin{aligned} 2- (a + b)(a + b') &= a.a + a.b' + a.b + b.b' \\ &= a + a.b' + a.b + 0 \\ &= a + a.(b' + b) + 0 \\ &= a + a.1 + 0 \\ &= a + a = a \end{aligned}$$



More Examples

- Show that;

(a) $ab + ab'c = ab + ac$

(b) $(a + b)(a + b' + c) = a + bc$

(a) $ab + ab'c = a(b + b'c)$
 $= a((b+b').(b+c)) = a(b+c) = ab + ac$

(b) $(a + b)(a + b' + c)$
 $= (a.a + a.b' + a.c + ab + b.b' + bc)$
 $= \dots$



DeMorgan's Theorem

$$(a) \ (a + b)' = a' b'$$

$$(b) \ (ab)' = a' + b'$$

Generalized DeMorgan's Theorem

$$(a) \ (a + b + \dots z)' = a' b' \dots z'$$

$$(b) \ (a.b \dots z)' = a' + b' + \dots z'$$



DeMorgan's Theorem

- $F = ab + c'd'$
 - $F' = ??$
-
- $F = ab + c'd' + b'd$
 - $F' = ??$



DeMorgan's Theorem

Show that. $(a + b.c)' = a'.b' + a'.c$



More *DeMorgan's* example

Show that: $(a(b + z(x + a')))' = a' + b' (z' + x')$

$$\begin{aligned}(a(b + z(x + a')))' &= a' + (b + z(x + a'))' \\&= a' + b' (z(x + a'))' \\&= a' + b' (z' + (x + a'))' \\&= a' + b' (z' + x'(a'))' \\&= a' + b' (z' + x'a) \\&= a' + b' z' + b'x'a \\&= (a' + b'x'a) + b' z' \\&= (a' + b'x')(a + a') + b' z' \\&= a' + b'x' + b' z' \\&= a' + b' (z' + x')\end{aligned}$$



More Examples

$$(a(b + c) + a'b)' = b'(a' + c')$$

$$ab + a'c + bc = ab + a'c$$

$$(a + b)(a' + c)(b + c) = (a + b)(a' + c)$$