


# Digital Logic Design

# Digital Signals

- Digital Signals have two basic states:
  - 1 (logic “high”, or H, or “on”)
  - 0 (logic “low”, or L, or “off”)
- Digital values are in a *binary* format.  
Binary means 2 states.
- A good example of binary is a light (only on or off) ON

- Strings of binary digits (“bits”)
  - One bit can store a number from 0 to 1
  - $n$  bits can store numbers from 0 to  $2^n$
- Positional representation
- Each digit represents a power of 2

So 101 binary is

$$1 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0$$

or

$$1 \cdot 4 + 0 \cdot 2 + 1 \cdot 1 = 5$$

# Converting Binary to Decimal

- multiply digit by power of 2
- Just like a decimal number is represented

7	6	5	4	3	2	1	0
$2^7$	$2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$
128	64	32	16	8	4	2	1

**What is 10011100 in decimal?**

1	0	0	1	1	1	0	0
---	---	---	---	---	---	---	---

$$128 + 0 + 0 + 16 + 8 + 4 + 0 + 0 = 156$$

# Binary

**In Binary, there are only 0's and 1's. These numbers are called “Base-2” ( Example:  $010_2$ )**

Binary to Decimal

Base 2 = Base 10

000 = 0

001 = 1

010 = 2

011 = 3

100 = 4

101 = 5

110 = 6

111 = 7

**We count in “Base-10”  
(0 to 9)**

# Binary as a Voltage

Voltages are used to represent logic values:


A voltage present (called  $V_{cc}$  or  $V_{dd}$ ) = 1

Zero Volts or ground (called gnd or  $V_{ss}$ ) = 0

A simple switch can provide a logic high or a logic low.
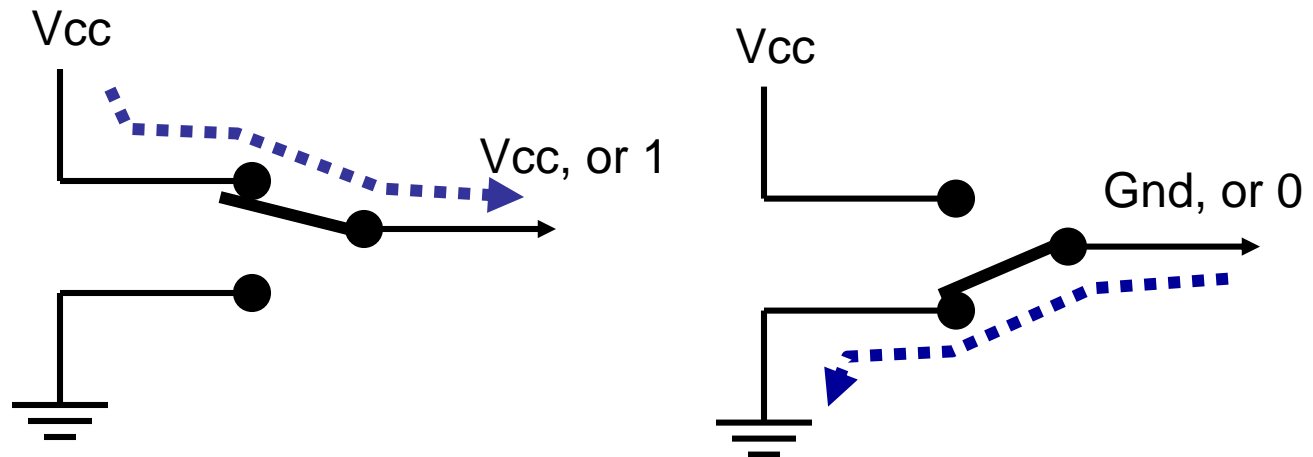
# A Simple Switch

- Here is a simple switch used to provide a logic value:



There are other ways to connect a switch.

# Digital Logic


- Basic Digital logic is based on 3 primary functions (the basic gates):
  - AND
  - OR
  - NOT



# The AND function

- The AND function:
  - If all the inputs are high the output is high
  - If any input is low, the output is low
- “If this input AND this input are high, the output is high”


# AND Logic Symbol

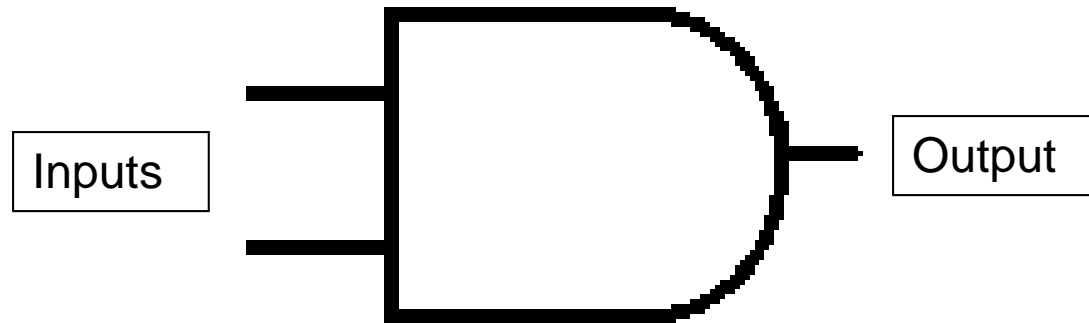


If both inputs are 1, the output is 1

If any input is 0, the output is 0


# AND Logic Symbol

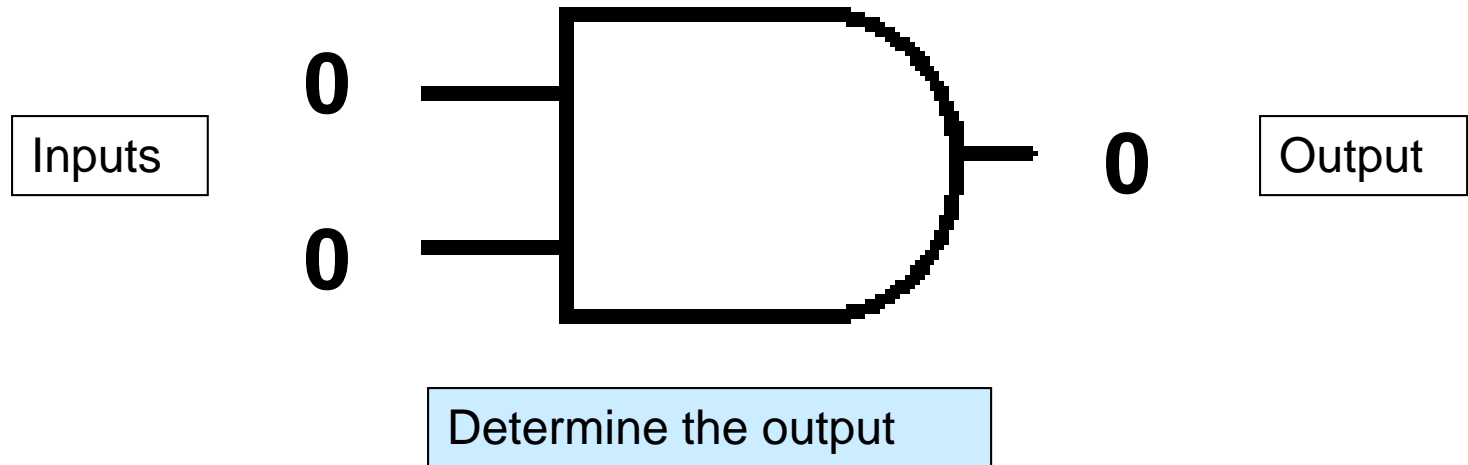

# AND Logic Symbol

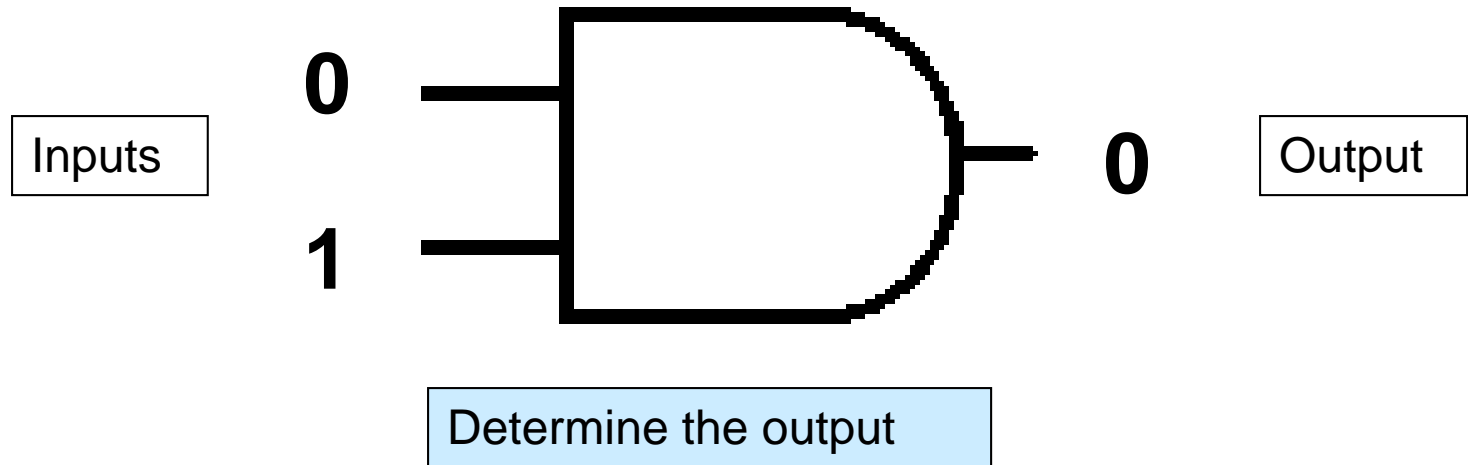

# AND Logic Symbol

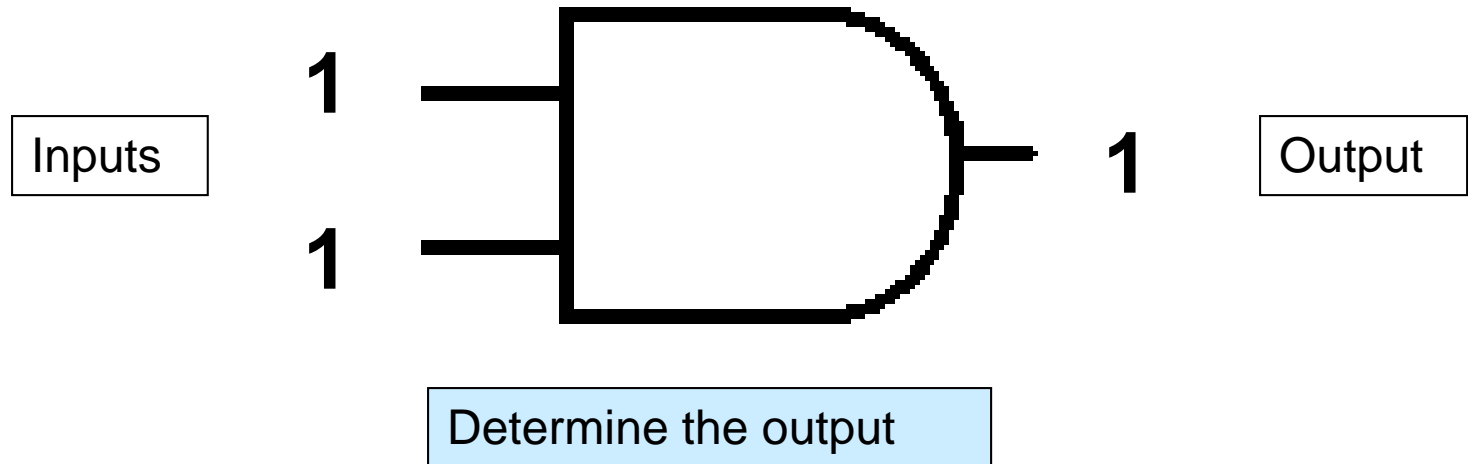



# AND Truth Table

- To help understand the function of a digital device, a Truth Table is used:

Every possible input combination	Input		Output
	0	0	0
	0	1	0
	1	0	0
	1	1	1
AND Function			
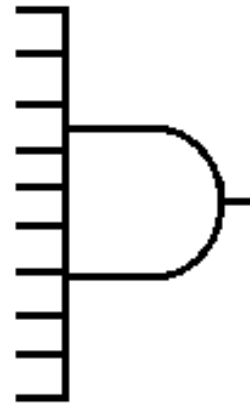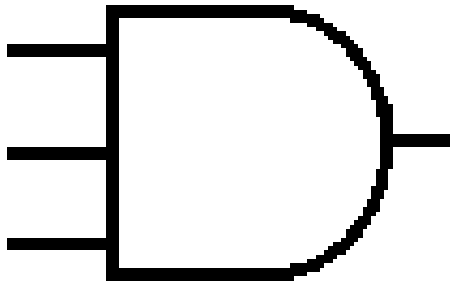
# AND Gates

- It is possible to have AND gates with more than 2 inputs. The same logic rules apply
  - “if any input...”




# The OR function

- The OR function:
  - if any input is high, the output is high
  - if all inputs are low, the output is low
- “If this input OR this input is high, the output is high”




# OR Logic Symbol

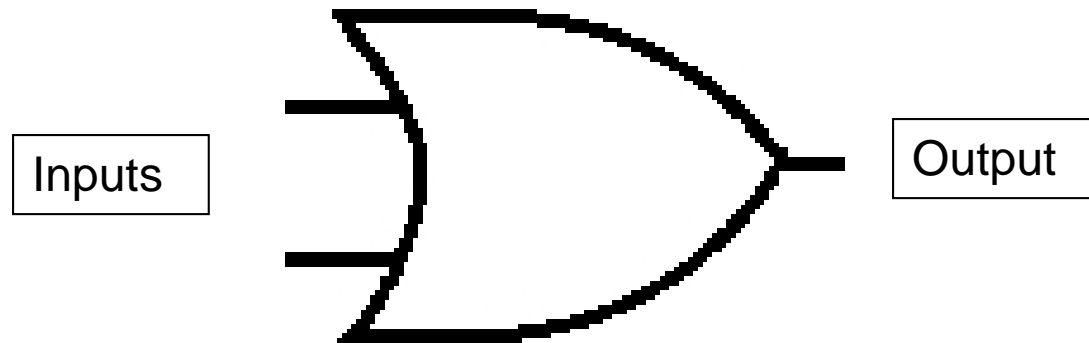

If any input is 1, the output is 1


If all inputs are 0, the output is 0

# OR Logic Symbol

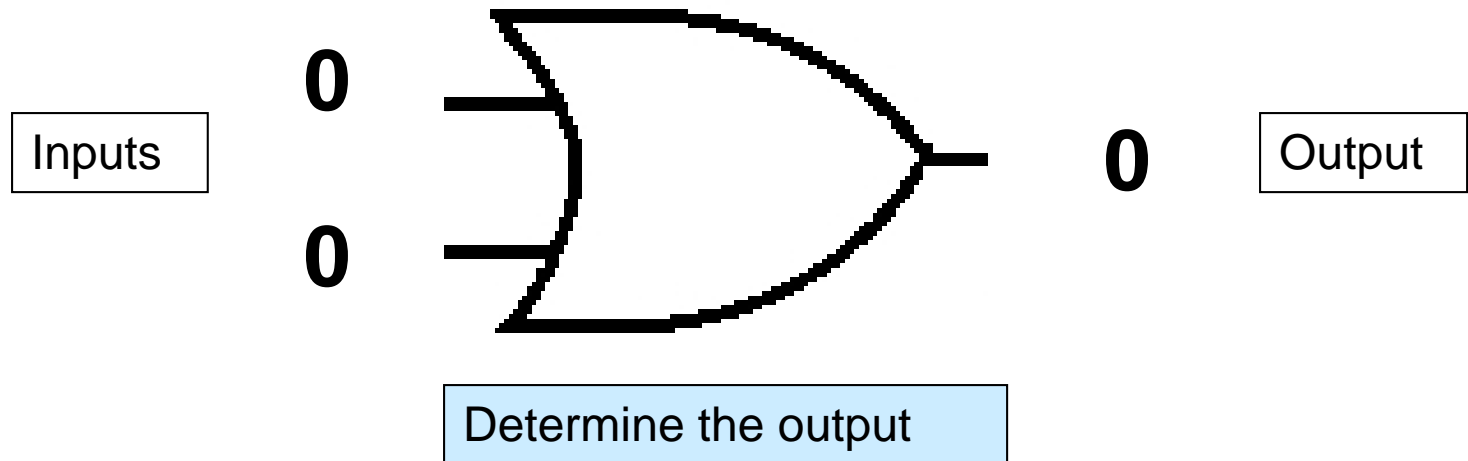


Animated Slide

# OR Logic Symbol

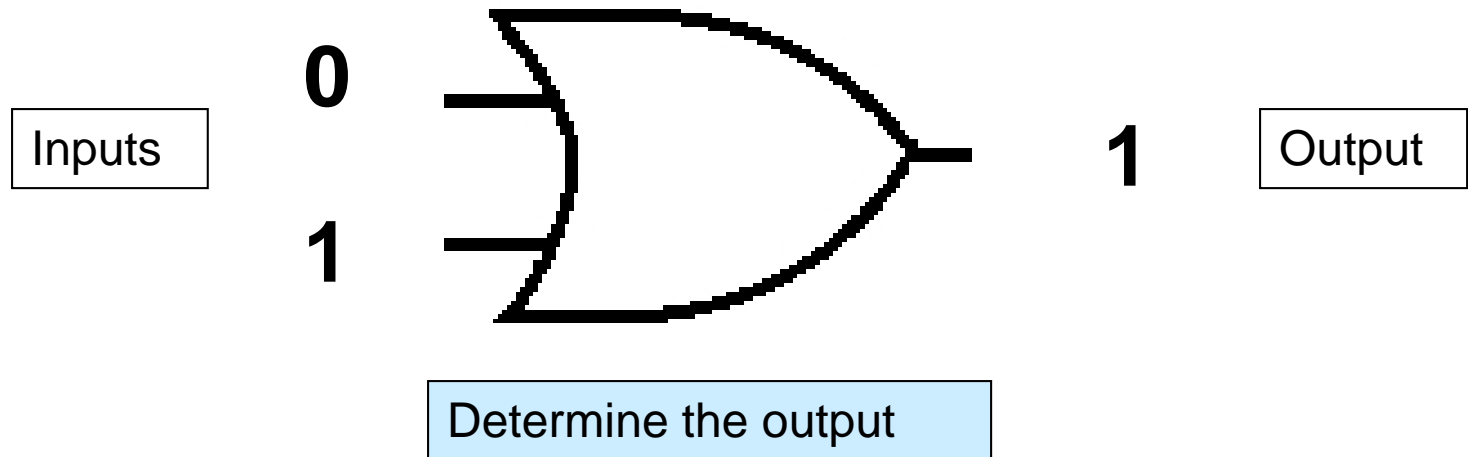

Animated Slide

# OR Logic Symbol

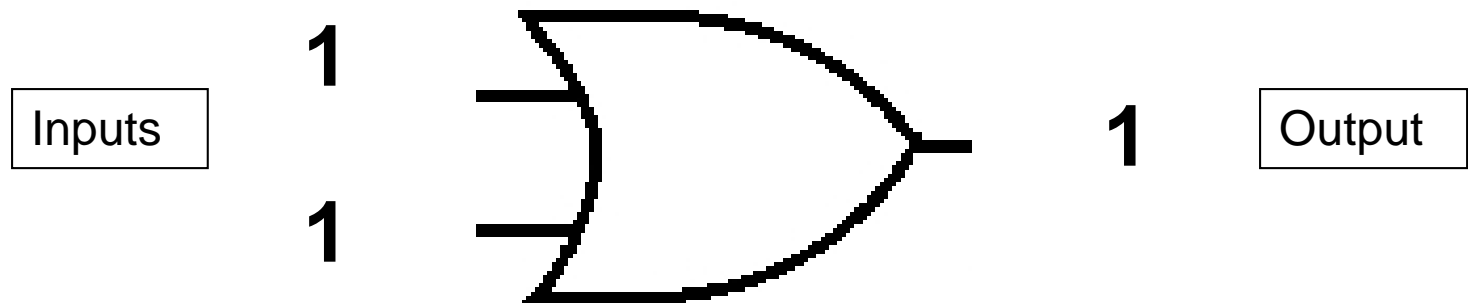

Determine the output

Animated Slide

# OR Truth Table

- Truth Table


Input		Output
0	0	0
0	1	1
1	0	1
1	1	1

**OR Function**

# The NOT function

- The NOT function:
  - If any input is high, the output is low
  - If any input is low, the output is high
- “The output is the opposite state of the input”
- The NOT function is often called INVERTER


# NOT Logic Symbol

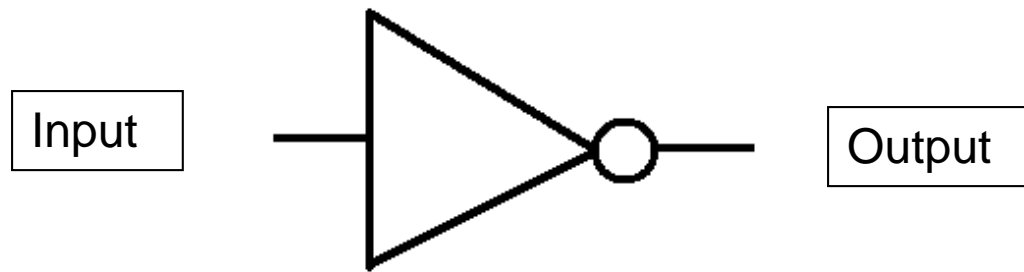

If the input is 1, the output is 0

If the input is 0, the output is 1

# NOT Logic Symbol

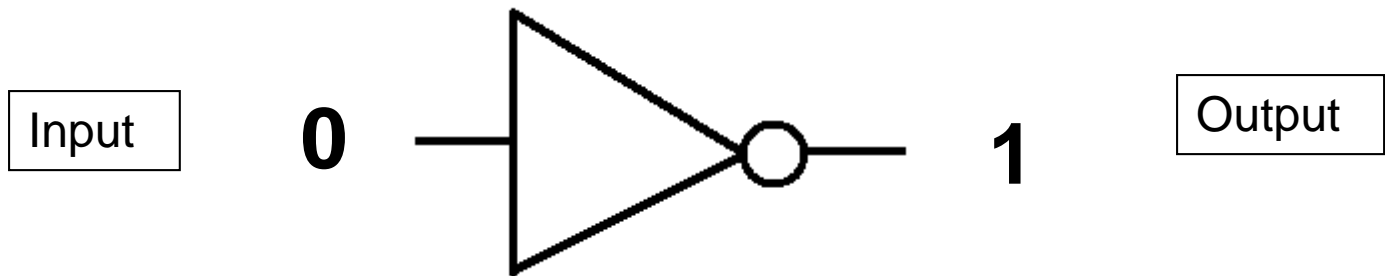


Determine the output

Animated Slide



# NOT Logic Symbol

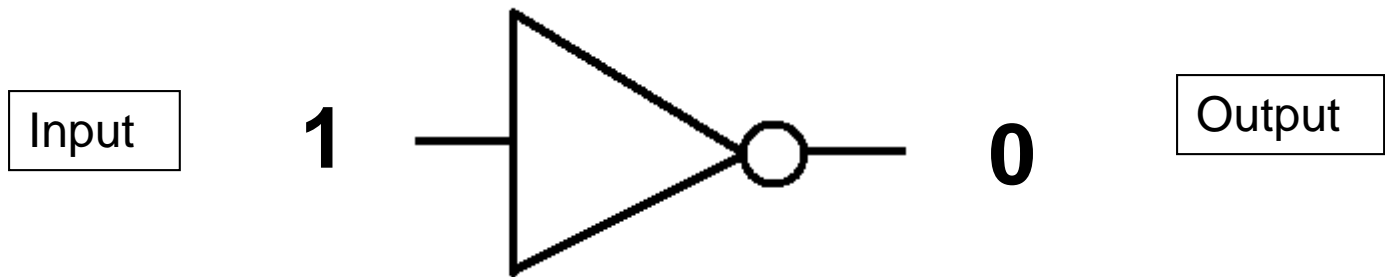

Determine the output

Animated Slide

# NOT Truth Table

- Truth Table

<b>Input</b>	<b>Output</b>
<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>


**NOT Function**

# Combinational Logic

- A circuit that utilizes more than 1 logic function has Combinational Logic.
- As an example, if a circuit has an AND gate connected to an Inverter gate, this circuit has combinational logic.

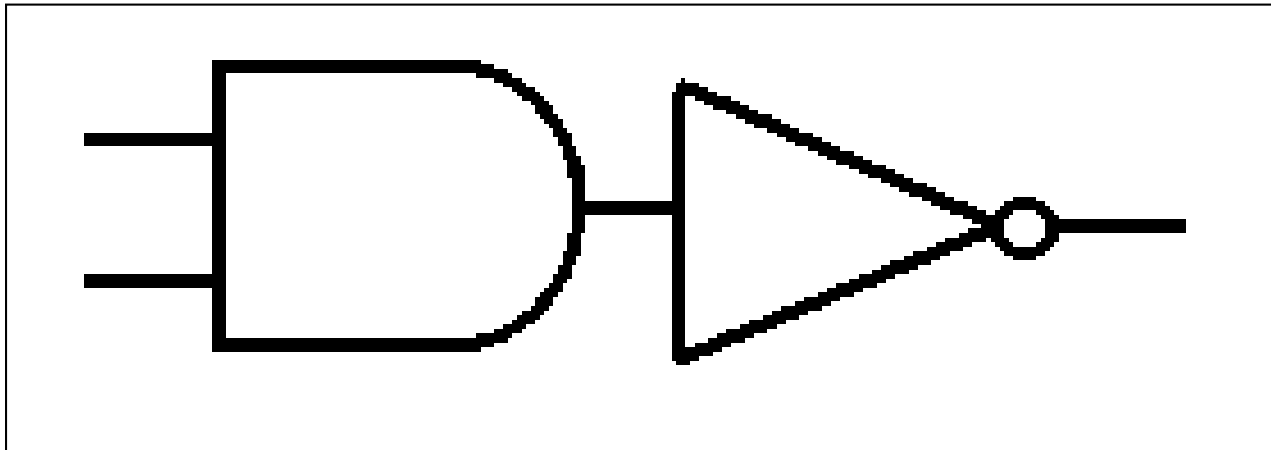
# Combinational logic

- How would you describe the output of this combinational logic circuit?


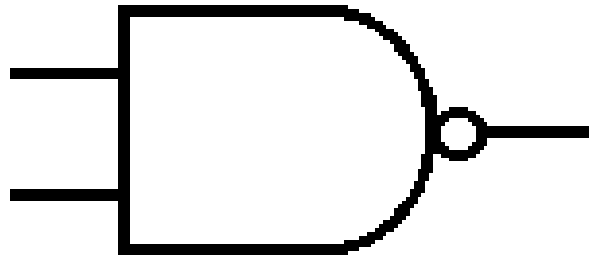
# NAND Gate


- The NAND gate is the combination of an NOT gate with an AND gate.



The Bubble in front of the gate is an inverter.

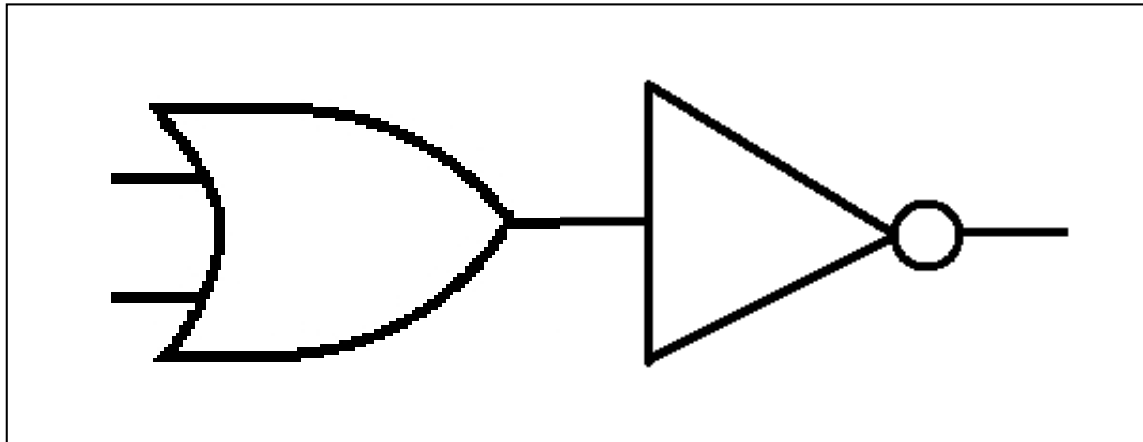
# Combinational logic

- How would you describe the output of this combinational logic circuit?


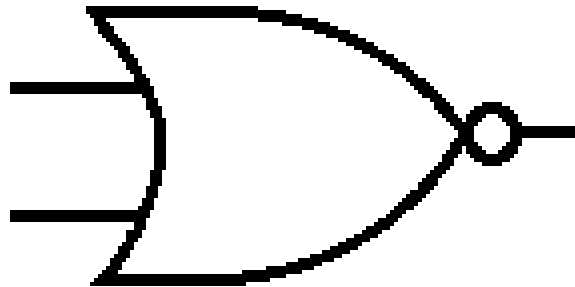
# NOR gate

- The NOR gate is the combination of the NOT gate with the OR gate.



The Bubble in front of the gate is an inverter.

# NAND and NOR gates

- The NAND and NOR gates are very popular as they can be connected in more ways than the simple AND and OR gates.




# Basic Digital Chips

- Digital Electronics devices are usually in a chip format.
- The chip is identified with a part number or a model number.
- A standard series starts with numbers 74, 4, or 14.
  - 7404 is an inverter
  - 7408 is an AND
  - 7432 is an OR
  - 4011B is a NAND

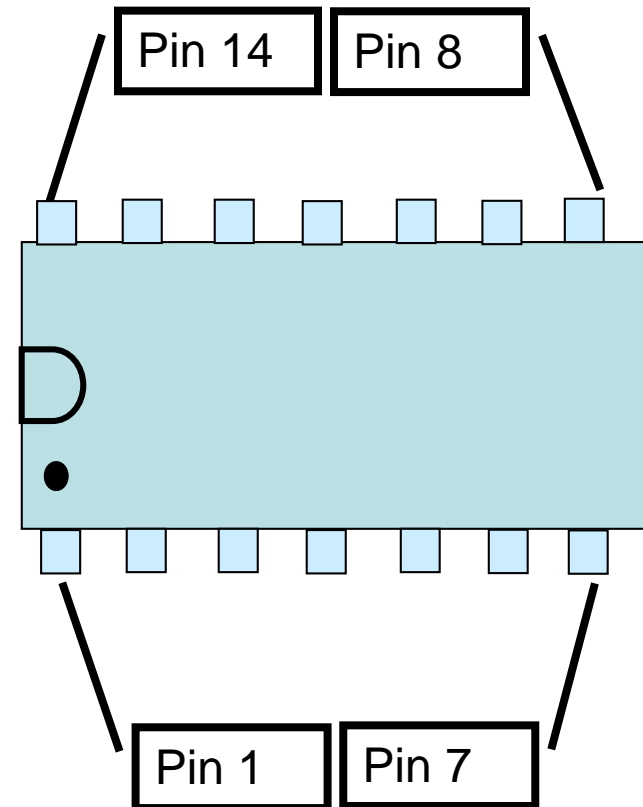
# Chips

- Basic logic chips often come in 14-pin packages.
- Package sizes and styles vary.
- Pin 1 is indicated with a dot or half-circle
- Numbers are read counter-clockwise from pin 1 (viewed from the top)


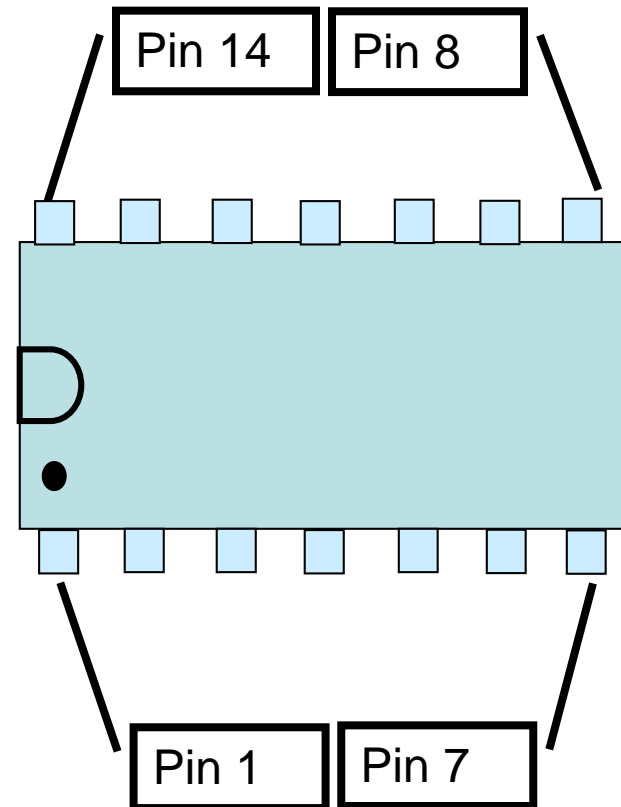
# Chips

- Chips require a voltage to function
- Vcc is equal to 5 volts and is typically pin 14
- Ground is typically pin 7




# Chips – Specification Sheet

## MC14011B

### Quad 2-Input NAND Gate


Voltage

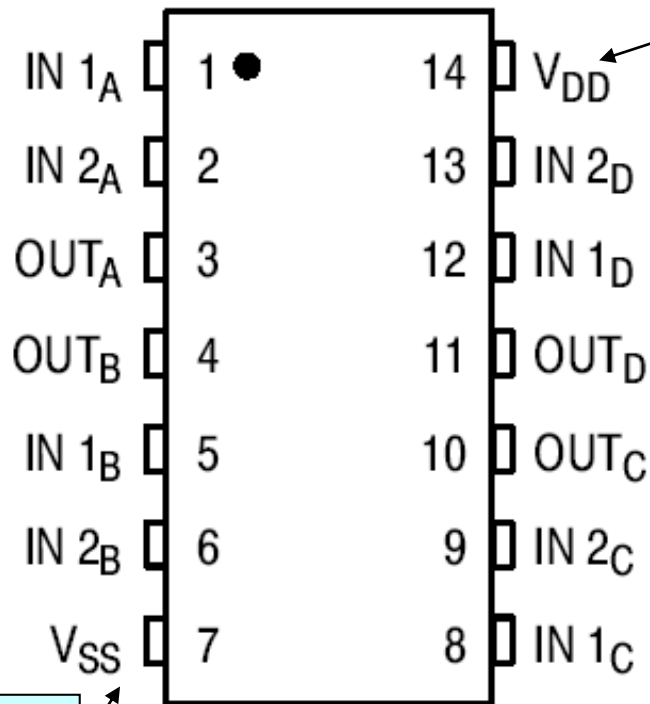


Ground

The voltage and ground pins must be connected for the device to function. Check the specification sheet to make sure.

# Chips – Specification Sheet

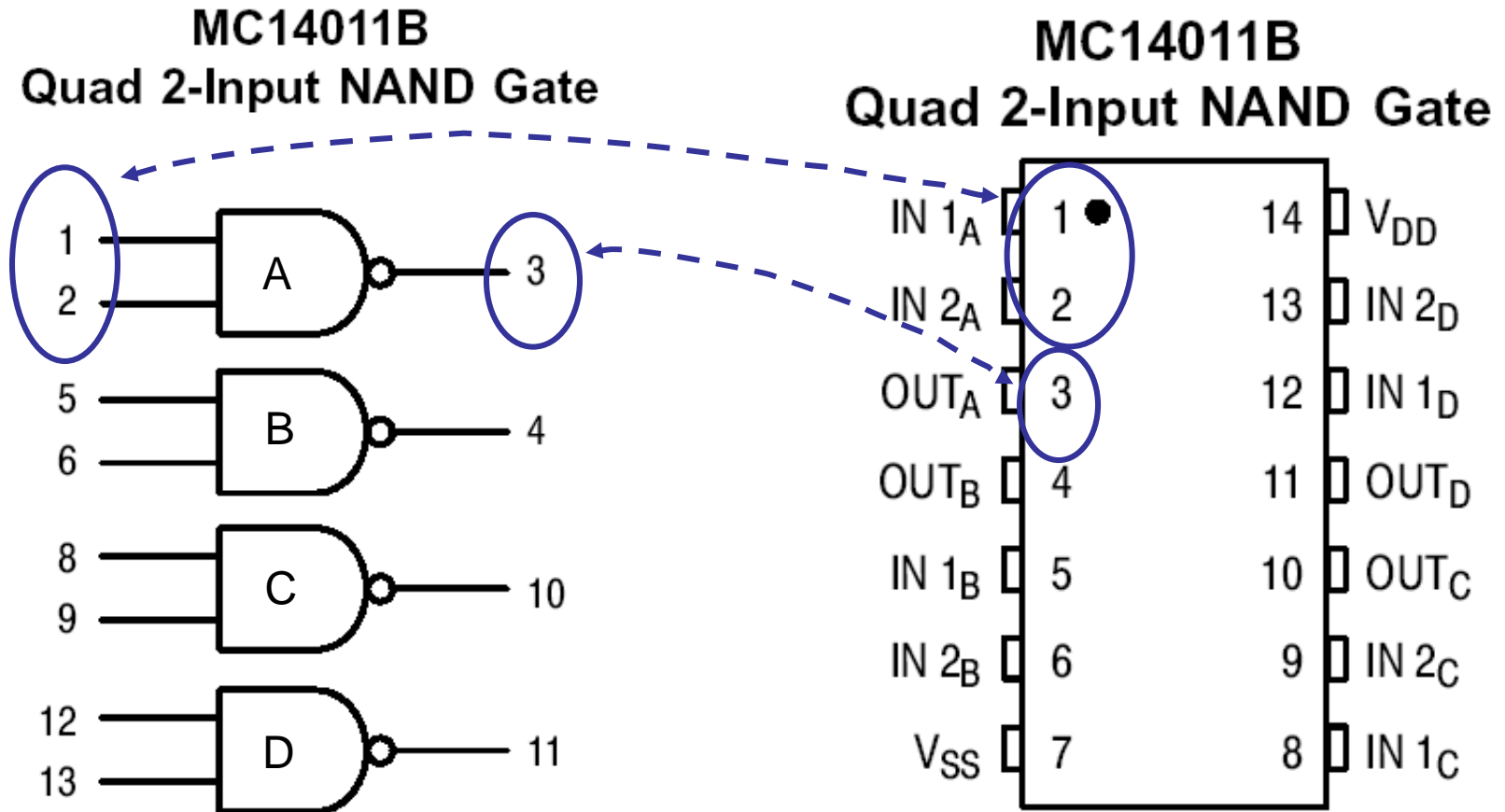


# Wiring a chip

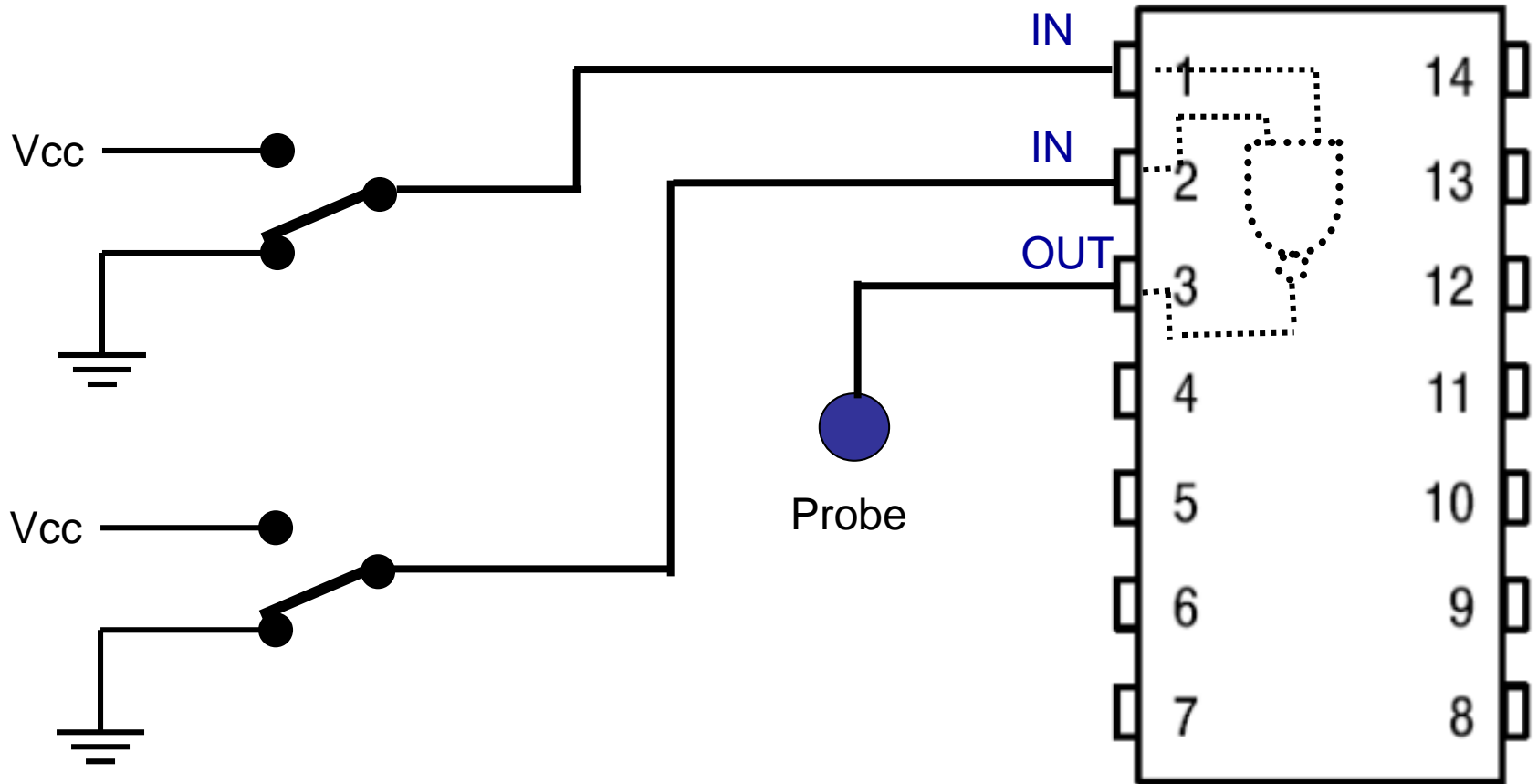

# More Two-Input Logic Gates


## XOR

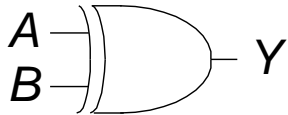

$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


## NAND

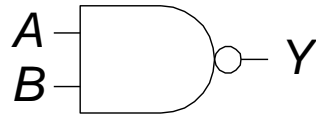

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


## NOR

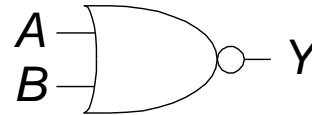

$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

## XNOR

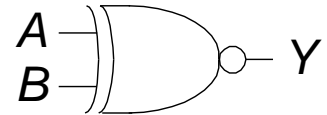

$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

# Exclusive OR

- Exclusive OR
- Symbol is  $\oplus$ 
  - Plus in a circle




$$F = X\bar{Y} + \bar{X}Y$$
$$= X \oplus Y$$

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	0




# Others

AND-OR-INVERT  
(AOI)

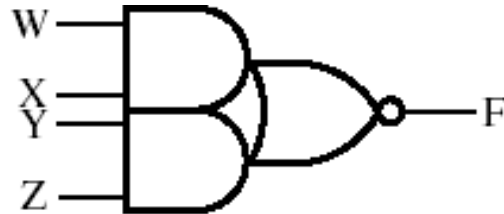

$$F = \overline{WX + YZ}$$

OR-AND -INVERT  
(OAI)

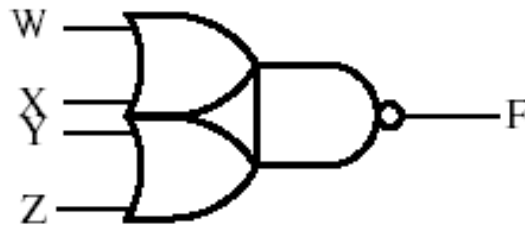

$$F = \overline{(W + X)(Y + Z)}$$

AND-OR  
(AO)



$$F = WX + YZ$$


OR-AND  
(OA)



$$F = (W + X)(Y + Z)$$

# Multiple-Input Logic Gates


## NOR3

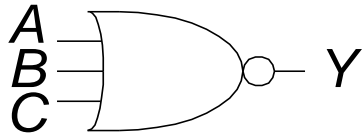

$$Y = \overline{A+B+C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

## AND4

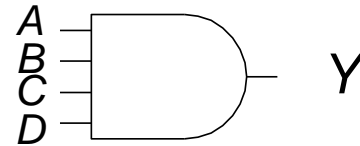




$$Y = ABCD$$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


# NAND is Universal

\*Can express any Boolean Function


\*Equivalents below

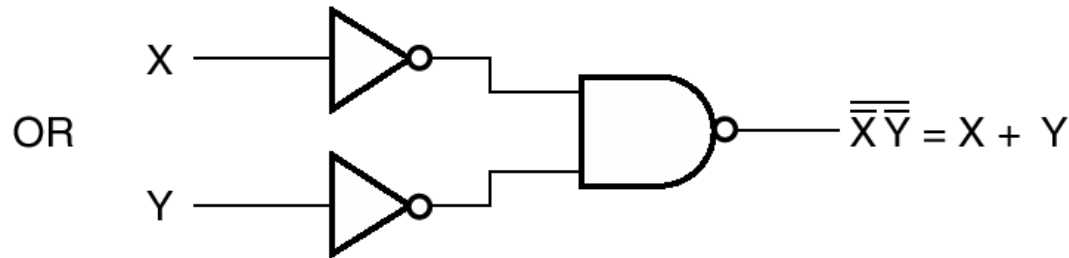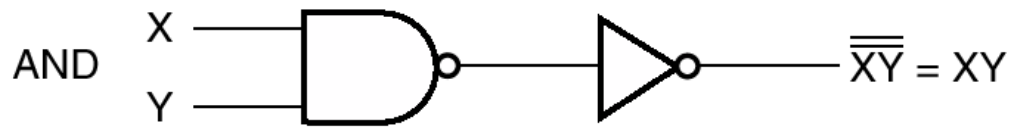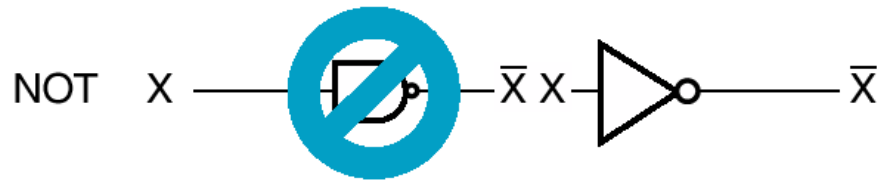


# Using NAND as Invert-OR

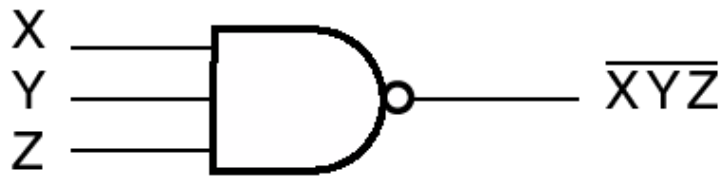

(a) AND - NOT

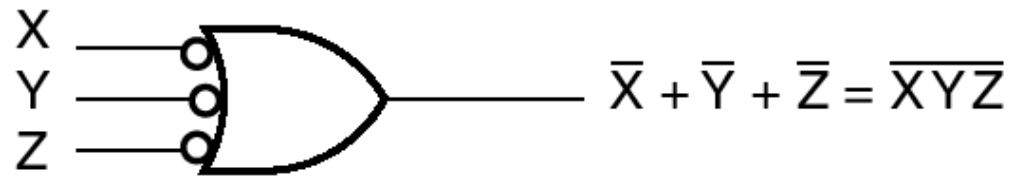

(b) NOT - OR

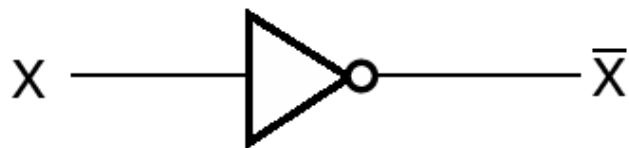

(c) NOT

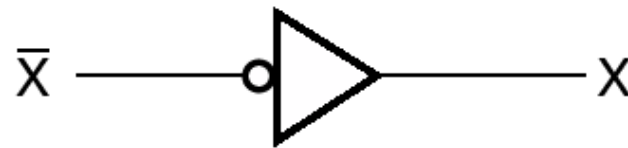


Fig. 2-28 Alternative Graphics Symbols for NAND and NOT Gates

✳️Also reverse inverter diagram for clarity

# NOR Also Universal

## \*Dual of NAND

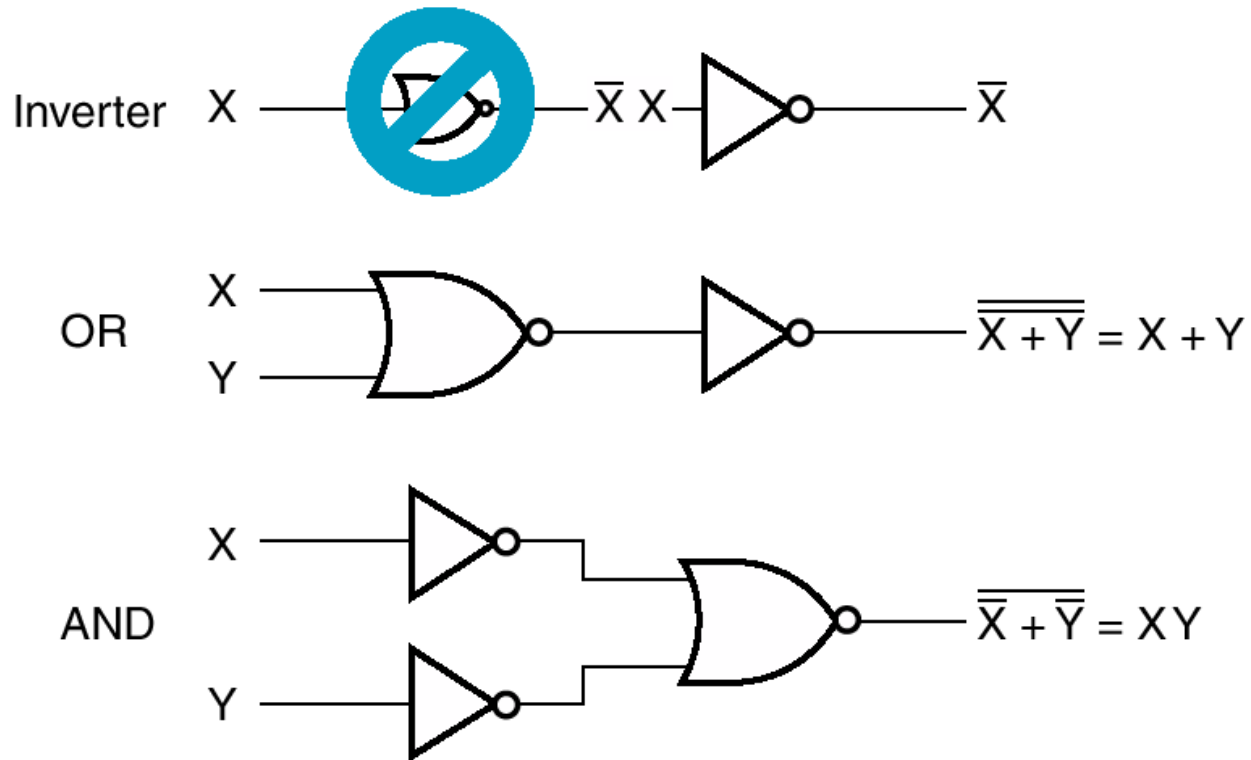


Fig. 2-33 Logic Operations with NOR Gates

# Representation: Schematic

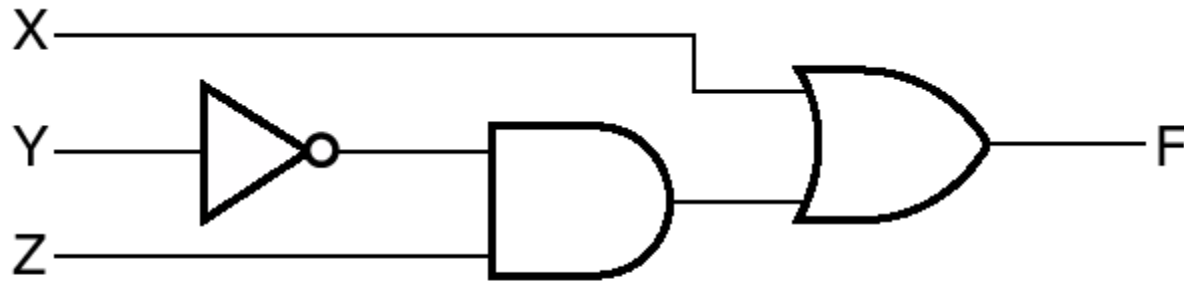


Fig. 2-3 Logic Circuit Diagram for  $F = X + \overline{Y}Z$

# Representation: Boolean Algebra

$$F = X + \bar{Y}Z$$

\* $2^n$  rows:


\*where  $n$  # of variables

**TABLE 2-2**  
**Truth Table**  
**for the Function  $F = X + \bar{Y}Z$**

<b>X</b>	<b>Y</b>	<b>Z</b>	<b>F</b>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1
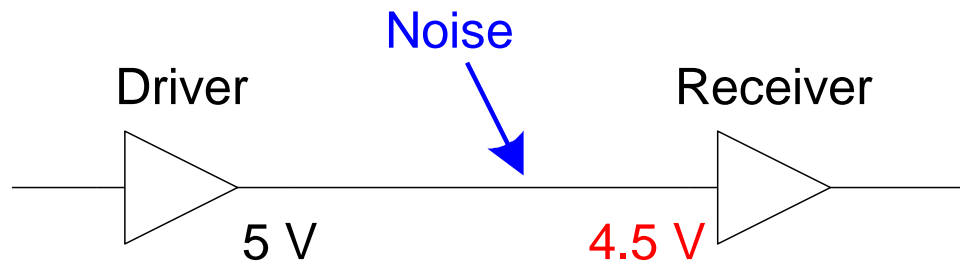
# What is Noise?

- Anything that degrades the signal
  - E.g., resistance, power supply noise, coupling to neighboring wires, etc.
- Example: a gate (driver) could output a 5 volt signal but, because of resistance in a long wire, the signal could arrive at the receiver with a degraded value, for example, 4.5 volts






# The Static Discipline

- ✱ Given logically valid inputs, every circuit element must produce logically valid outputs
- ✱ Discipline ourselves to use limited ranges of voltages to represent discrete values

# Noise Margins

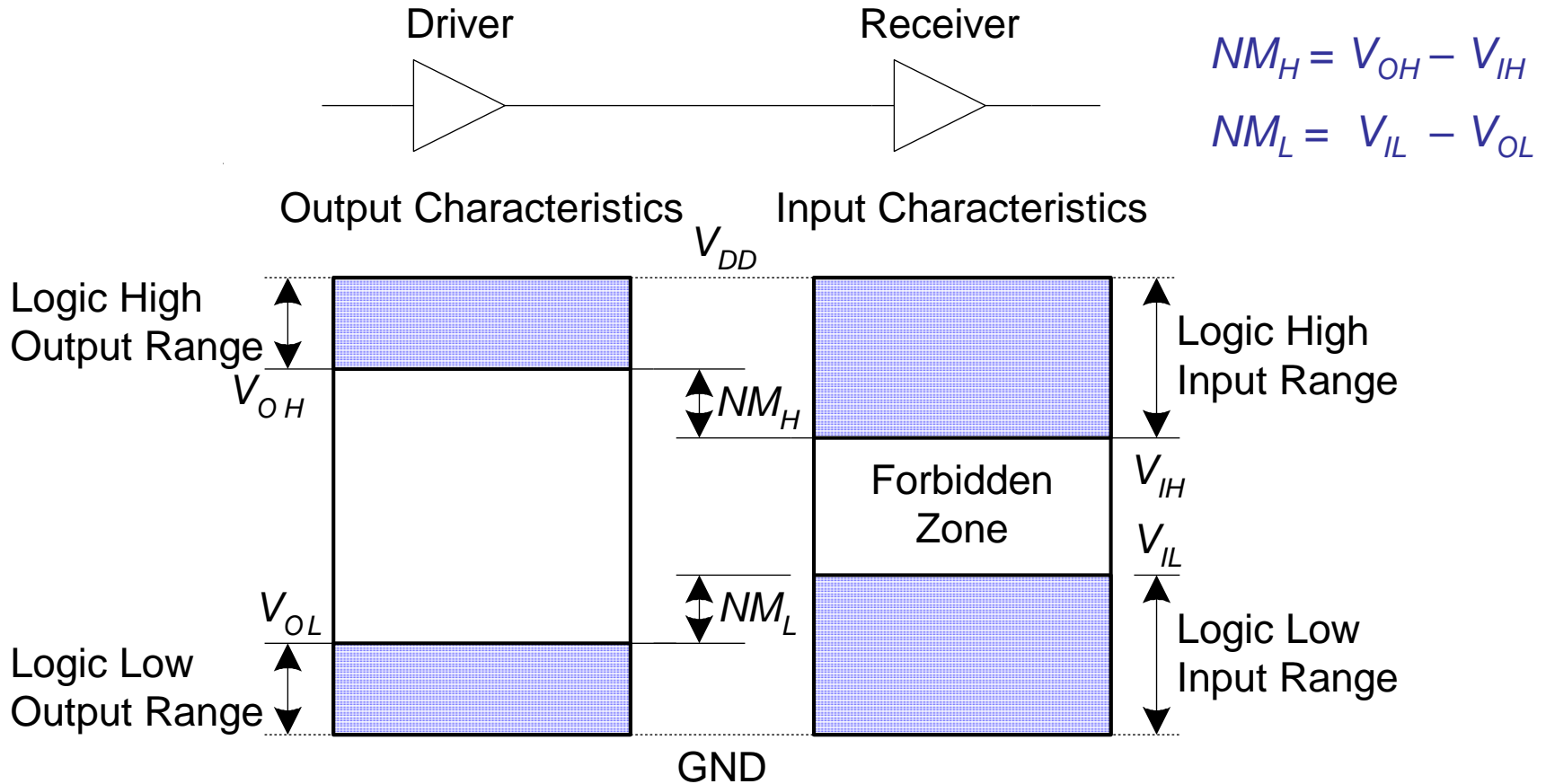

# Logic Family Examples

Logic Family	$V_{DD}$	$V_{IL}$	$V_{IH}$	$V_{OL}$	$V_{OH}$
TTL	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5 - 6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
LVC MOS	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7

# Identities

- Use identities to manipulate functions
- You can use distributive law ...

$$X + YZ = (X + Y)(X + Z)$$

... to transform from  $F = X + \bar{Y}Z$   
to

$$F = (X + \bar{Y})(X + Z)$$

# Table of Identities

□ **TABLE 2-3**  
**Basic Identities of Boolean Algebra**

1.	$X + 0 = X$	2.	$X \cdot 1 = X$	
3.	$X + 1 = 1$	4.	$X \cdot 0 = 0$	
5.	$X + X = X$	6.	$X \cdot X = X$	
7.	$X + \bar{X} = 1$	8.	$X \cdot \bar{X} = 0$	
9.	$\overline{\bar{X}} = X$			
10.	$X + Y = Y + X$	11.	$XY = YX$	Commutative
12.	$X + (Y + Z) = (X + Y) + Z$	13.	$X(YZ) = (XY)Z$	Associative
14.	$X(Y + Z) = XY + XZ$	15.	$X + YZ = (X + Y)(X + Z)$	Distributive
16.	$\overline{X + Y} = \bar{X} \cdot \bar{Y}$	17.	$\overline{X \cdot Y} = \bar{X} + \bar{Y}$	DeMorgan's

# Duals

- \* Left and right columns are *duals*
- \* Replace AND and OR, 0s and 1s

□ **TABLE 2-3**  
**Basic Identities of Boolean Algebra**

1. $X + 0 = X$	2. $X \cdot 1 = X$	
3. $X + 1 = 1$	4. $X \cdot 0 = 0$	
5. $X + X = X$	6. $X \cdot X = X$	
7. $X + \bar{X} = 1$	8. $X \cdot \bar{X} = 0$	
9. $\overline{\bar{X}} = X$		
10. $X + Y = Y + X$	11. $XY = YX$	Commutative
12. $X + (Y + Z) = (X + Y) + Z$	13. $X(YZ) = (XY)Z$	Associative
14. $X(Y + Z) = XY + XZ$	15. $X + YZ = (X + Y)(X + Z)$	Distributive
16. $\overline{X + Y} = \bar{X} \cdot \bar{Y}$	17. $\overline{X \cdot Y} = \bar{X} + \bar{Y}$	DeMorgan's

# Single Variable Identities

$$1. \quad X + 0 = X$$

$$2. \quad X \cdot 1 = X$$

$$3. \quad X + 1 = 1$$

$$4. \quad X \cdot 0 = 0$$

$$5. \quad X + X = X$$

$$6. \quad X \cdot X = X$$

$$7. \quad X + \overline{X} = 1$$

$$8. \quad X \cdot \overline{X} = 0$$

$$9. \quad \overline{\overline{X}} = X$$

# Commutativity

\*Operation is independent of order of variables

$$10. \quad X + Y = Y + X$$

$$11. \quad XY = YX$$



# Associativity

✱Independent of order in which we group

$$12. \quad X + (Y + Z) = (X + Y) + Z$$

$$13. \quad X(YZ) = (XY)Z$$

✱So can also be written as  $X + Y + Z$   
and  $XYZ$

# Distributivity

$$14. \quad X(Y + Z) = XY + XZ$$

$$15. \quad X + YZ = (X + Y)(X + Z)$$

✱ Can substitute arbitrarily large algebraic expressions for the variables


- Distribute an operation over the entire expression

# DeMorgan's Theorem

\*Used a lot



\*NOR  $\rightarrow$  invert, then AND
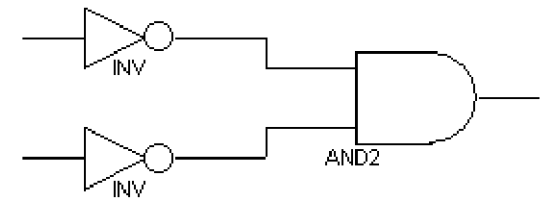
$$16. \quad \overline{X + Y} = \bar{X} \cdot \bar{Y}$$



\*NAND  $\rightarrow$  invert, then OR
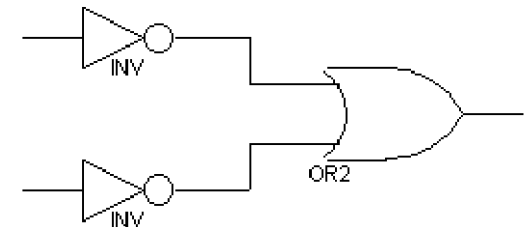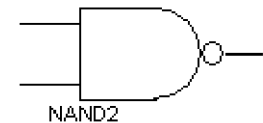
$$17. \quad \overline{X \cdot Y} = \bar{X} + \bar{Y}$$



# Truth Tables for DeMorgan's


A)	X	Y	$X + Y$	$\overline{X+Y}$	B )	X	Y	$\bar{X}$	$\bar{Y}$	$\bar{X} \cdot \bar{Y}$
	0	0	0	1		0	0	1	1	1
	0	1	1	0		0	1	1	0	0
	1	0	1	0		1	0	0	1	0
	1	1	1	0		1	1	0	0	0

$$16. \quad \overline{X+Y} = \bar{X} \cdot \bar{Y}$$

# Algebraic Manipulation

\*Consider function

$$F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$$

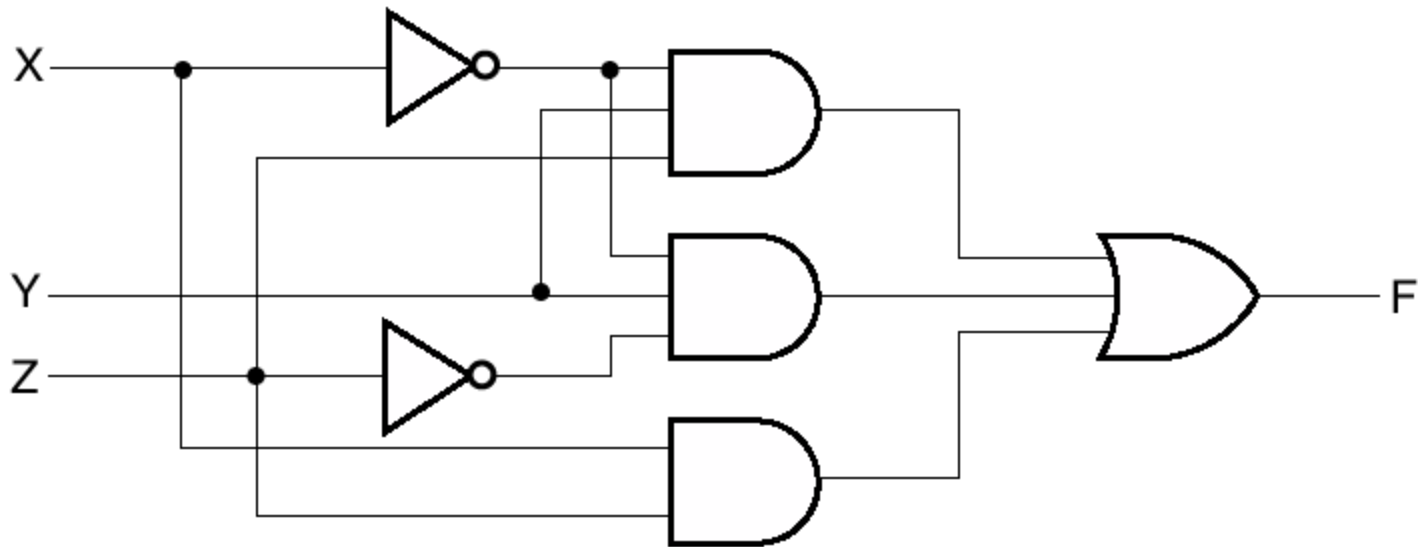

(a)  $F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$

# Simplify Function

$$F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$$

Apply

$$14. \quad X(Y + Z) = XY + XZ$$

$$F = \bar{X}Y(Z + \bar{Z}) + XZ$$

Apply

$$7. \quad X + \bar{X} = 1$$

$$F = \bar{X}Y \bullet 1 + XZ$$


Apply

$$2. \quad X \cdot 1 = X$$

$$F = \bar{X}Y + XZ$$


# Fewer Gates

$$F = \bar{X}Y + XZ$$

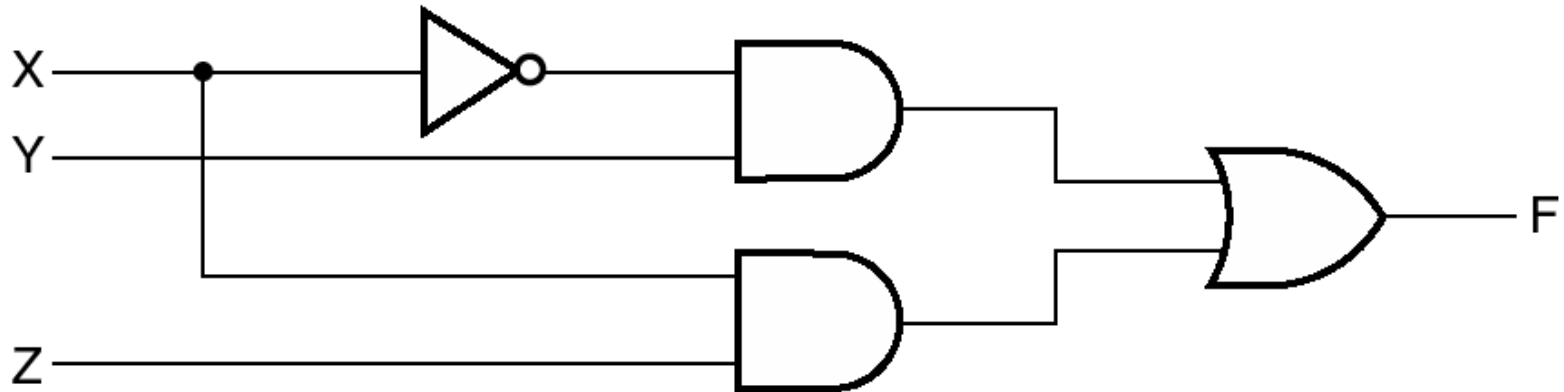

(b)  $F = \bar{X}Y + XZ$

Fig. 2-4 Implementation of Boolean Function with Gates

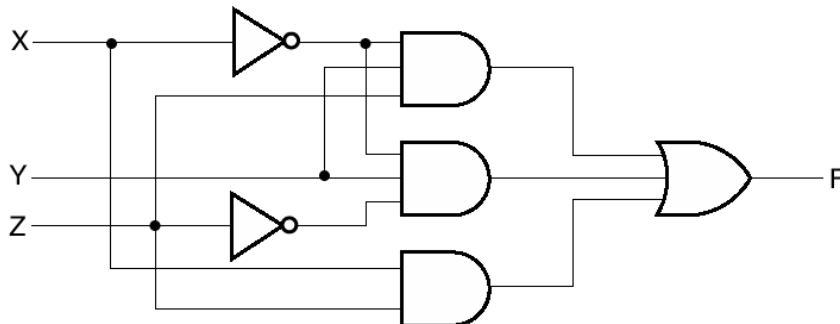

(a)  $F = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$

# Consensus Theorem

$$XY + \bar{X}Z + \textcircled{YZ} = XY + \bar{X}Z$$

- The third term is redundant
  - Can just drop
- Proof summary:
  - For third term to be true, Y & Z both must be 1
  - Then one of the first two terms is already 1!



# Standard Forms

- Definitions:
  - Product terms – AND  $\rightarrow \bar{A}BZ$
  - Sum terms – OR  $\rightarrow X + \bar{A}$
  - This is logical product and sum, not arithmetic

# Definition: Minterm

✱ Product term in which all variables appear once (complemented or not)

X	Y	Z	Product Term	Symbol	m <sub>0</sub>	m <sub>1</sub>	m <sub>2</sub>	m <sub>3</sub>	m <sub>4</sub>	m <sub>5</sub>	m <sub>6</sub>	m <sub>7</sub>
0	0	0	$\overline{X}\overline{Y}\overline{Z}$	m <sub>0</sub>	1	0	0	0	0	0	0	0
0	0	1	$\overline{X}\overline{Y}Z$	m <sub>1</sub>	0	1	0	0	0	0	0	0
0	1	0	$\overline{X}Y\overline{Z}$	m <sub>2</sub>	0	0	1	0	0	0	0	0
0	1	1	$\overline{X}YZ$	m <sub>3</sub>	0	0	0	1	0	0	0	0
1	0	0	$X\overline{Y}\overline{Z}$	m <sub>4</sub>	0	0	0	0	1	0	0	0
1	0	1	$X\overline{Y}Z$	m <sub>5</sub>	0	0	0	0	0	1	0	0
1	1	0	$XY\overline{Z}$	m <sub>6</sub>	0	0	0	0	0	0	1	0
1	1	1	$XYZ$	m <sub>7</sub>	0	0	0	0	0	0	0	1

# Number of Minterms

- For  $n$  variables, there will be  $2^n$  minterms
- Like binary numbers from 0 to  $2^n-1$
- Often numbered same way (with decimal conversion)

# Maxterms

- Sum term in which all variables appear once (complemented or not)

X	Y	Z	Sum Term	Symbol	M <sub>0</sub>	M <sub>1</sub>	M <sub>2</sub>	M <sub>3</sub>	M <sub>4</sub>	M <sub>5</sub>	M <sub>6</sub>	M <sub>7</sub>
0	0	0	$X+Y+Z$	M <sub>0</sub>	0	1	1	1	1	1	1	1
0	0	1	$X+Y+\bar{Z}$	M <sub>1</sub>	1	0	1	1	1	1	1	1
0	1	0	$X+\bar{Y}+Z$	M <sub>2</sub>	1	1	0	1	1	1	1	1
0	1	1	$X+\bar{Y}+\bar{Z}$	M <sub>3</sub>	1	1	1	0	1	1	1	1
1	0	0	$\bar{X}+Y+Z$	M <sub>4</sub>	1	1	1	1	0	1	1	1
1	0	1	$\bar{X}+Y+\bar{Z}$	M <sub>5</sub>	1	1	1	1	1	0	1	1
1	1	0	$\bar{X}+\bar{Y}+Z$	M <sub>6</sub>	1	1	1	1	1	1	0	1
1	1	1	$\bar{X}+\bar{Y}+\bar{Z}$	M <sub>7</sub>	1	1	1	1	1	1	1	0

# Minterm related to Maxterm

✱ Minterm and maxterm with same subscripts are complements

$$\overline{m}_j = M_j$$

✱ Example

$$\overline{m}_3 = \overline{\overline{X}YZ} = X + \overline{Y} + \overline{Z} = M_3$$

# Sum of Minterms

- OR all of the minterms of truth table row with a 1
  - “ON-set minterms”

X	Y	Z	F	$\bar{F}$
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

$$F = \bar{X}\bar{Y}Z + X\bar{Y}\bar{Z} + X\bar{Y}Z + XY\bar{Z} + XYZ$$

# Sum of Products

- Simplifying sum-of-minterms can yield a sum of products
- Difference is each term need not be a minterm
  - i.e., terms do not need to have all variables
- A bunch of ANDs and one OR


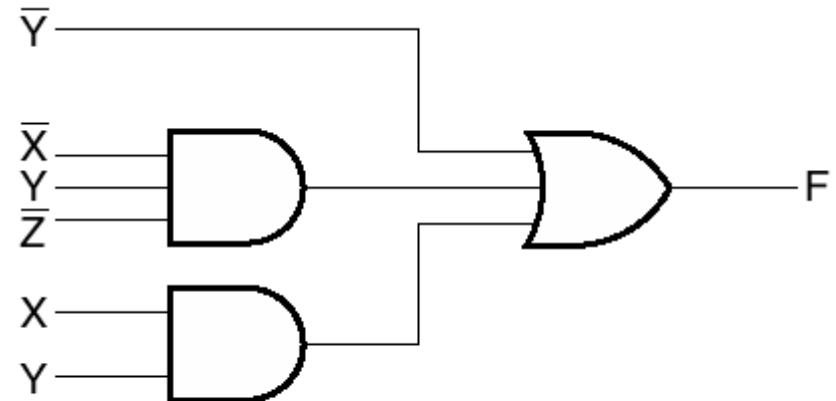


Fig. 2-5 Sum-of-Products Implementation

# Two-Level Implementation


\*Sum of products has 2 levels of gates

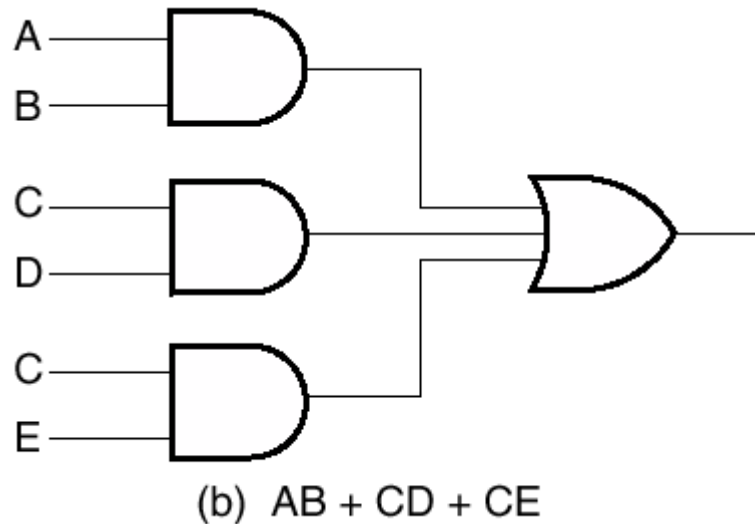


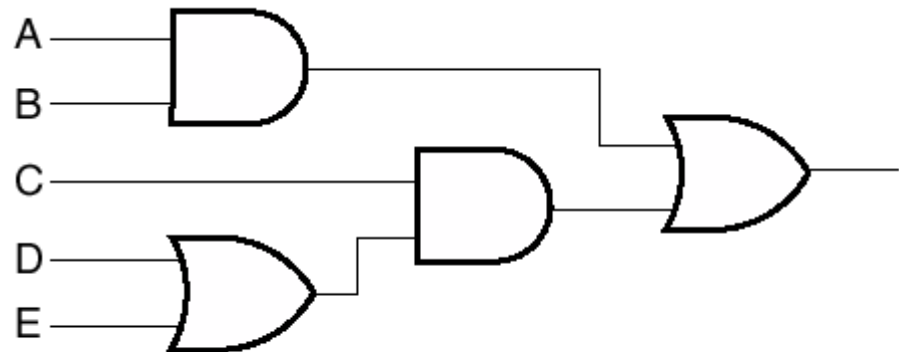
# More Levels of Gates?

- What's best?
  - Hard to answer
  - More gate delays
  - But maybe we only have 2-input gates
    - So multi-input ANDs and ORs have to be decomposed



(a)  $AB + C(D + E)$

# Complement of a Function

- \*Definition: 1s & 0s swapped in truth table
- \*Mechanical way to derive algebraic form
  - Take the dual
    - Recall: Interchange AND and OR, and 1s & 0s
  - Complement each literal

# Complement of F

- Not surprisingly, just sum of the other minterms
  - “OFF-set minterms”

- In this case

$$m_1 + m_3 + m_4 + m_6$$

X	Y	Z	F	$\bar{F}$
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

# Product of Maxterms

✱ Recall that maxterm is true except for its own case

✱ So  $M_1$  is only false for 001

X	Y	Z	Sum Term	Symbol	$M_0$	$M_1$	$M_2$	$M_3$	$M_4$	$M_5$	$M_6$	$M_7$
0	0	0	$X+Y+Z$	$M_0$	0	1	1	1	1	1	1	1
0	0	1	$X+Y+\bar{Z}$	$M_1$	1	0	1	1	1	1	1	1
0	1	0	$X+\bar{Y}+Z$	$M_2$	1	1	0	1	1	1	1	1
0	1	1	$X+\bar{Y}+\bar{Z}$	$M_3$	1	1	1	0	1	1	1	1
1	0	0	$\bar{X}+Y+Z$	$M_4$	1	1	1	1	0	1	1	1
1	0	1	$\bar{X}+Y+\bar{Z}$	$M_5$	1	1	1	1	1	0	1	1
1	1	0	$\bar{X}+\bar{Y}+Z$	$M_6$	1	1	1	1	1	1	0	1
1	1	1	$\bar{X}+\bar{Y}+\bar{Z}$	$M_7$	1	1	1	1	1	1	1	0

# Product of Maxterms

- Can express F as AND of all rows that should evaluate to 0

$$F = M_1 \bullet M_3 \bullet M_4 \bullet M_6$$

or

$$F = (X + Y + \bar{Z})(X + \bar{Y} + \bar{Z}) \\ (\bar{X} + Y + Z)(\bar{X} + \bar{Y} + Z)$$

X	Y	Z	F	$\bar{F}$
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

# Product of Sums

- Result: another standard form
- ORs followed by AND
  - Terms do not have to be maxterms

$$F = X(\bar{Y} + Z)(X + Y + \bar{Z})$$

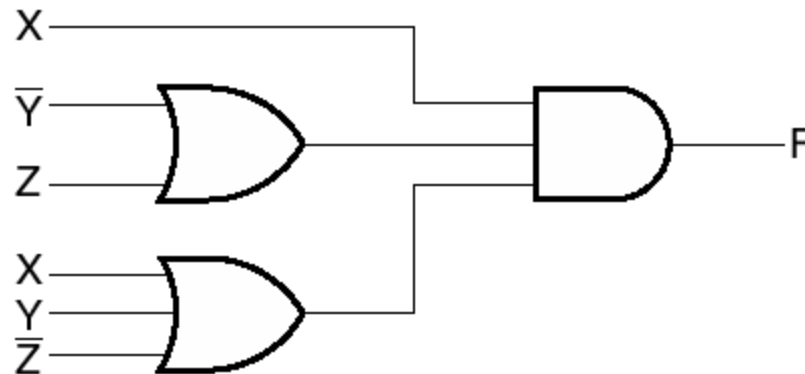


Fig. 2-7 Product-of-Sums Implementation