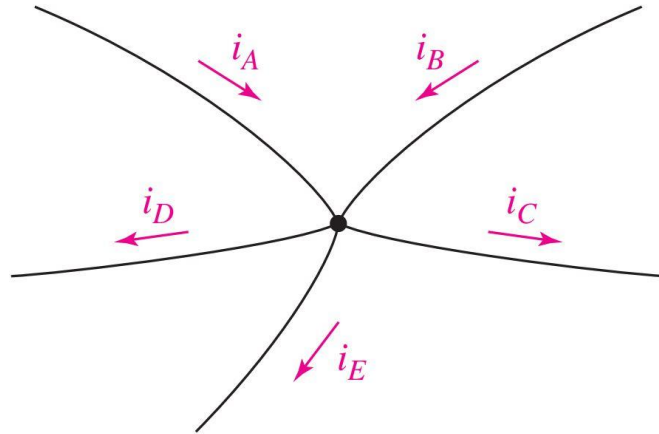


# Fundamentals of Electronics (ECN-102 )




## Tutorial 1(Chapter 1)

1. Referring to the below node compute:



- a)  $i_B$ , if  $i_A = 2\text{A}$ ,  $i_C = -1\text{A}$ ,  $i_D = 4\text{A}$  and  $i_E = 0\text{A}$
- b)  $i_A$ , if  $i_B = -2\text{A}$ ,  $i_C = 2\text{A}$ ,  $i_D = 1\text{A}$  and  $i_E = -3\text{A}$  using KCL



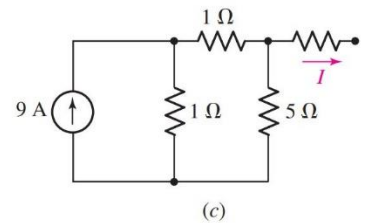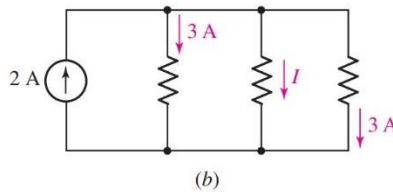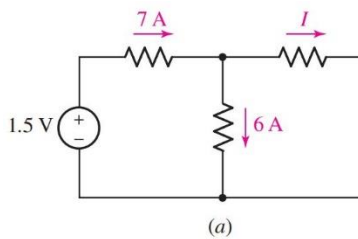2. Determine the current  $I$  in the below circuits:




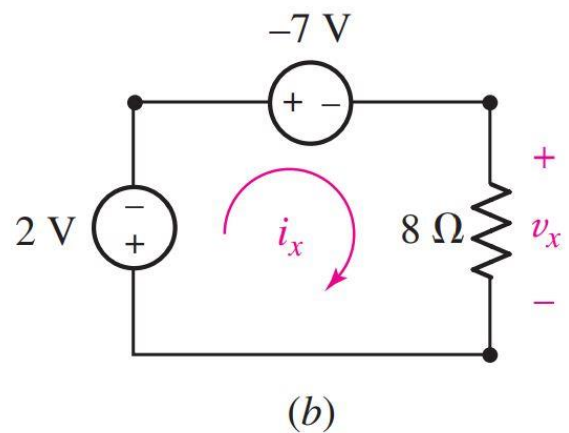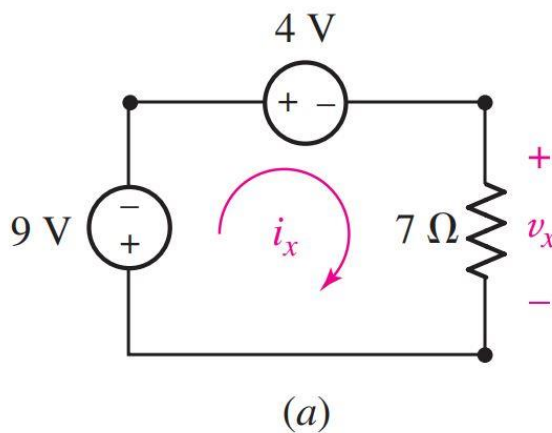3. In the following circuits determine voltage  $v_x$  and current  $i_x$  using KVL:




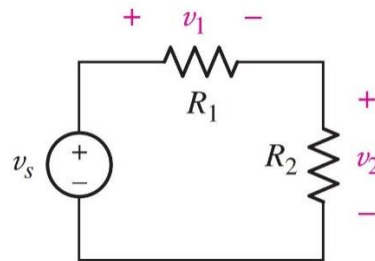4. Consider the simple circuit below. Derive the following expressions for voltages using KVL:


$$v_1 = v_s \frac{R_1}{R_1 + R_2} \quad \text{and} \quad v_2 = v_s \frac{R_2}{R_1 + R_2}$$



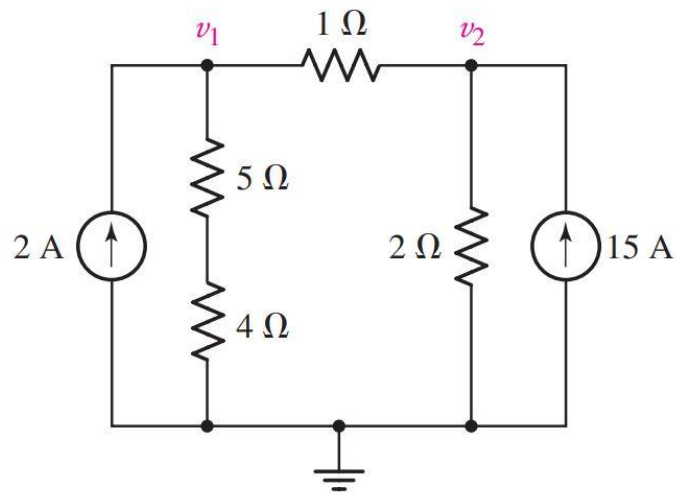
5. Using nodal analysis determine  $v_1$ - $v_2$  in the below circuit:



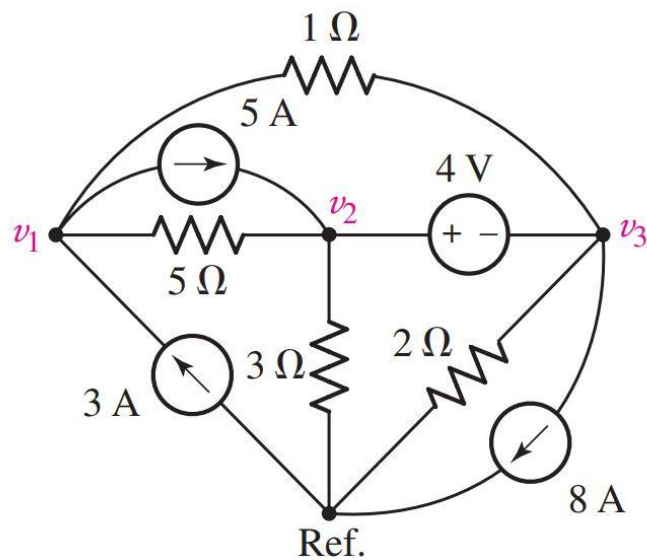
6. Determine the node voltages  $v_1$ ,  $v_2$  and  $v_3$  using super node technique:



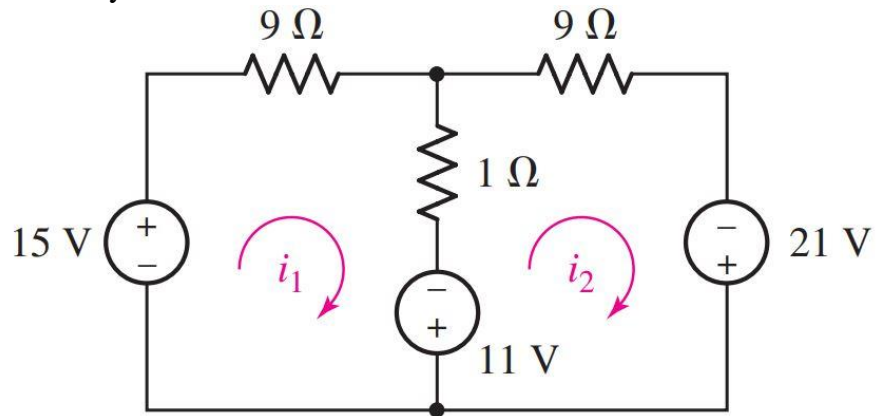
7. Using mesh analysis determine the mesh currents labelled in the below circuit:



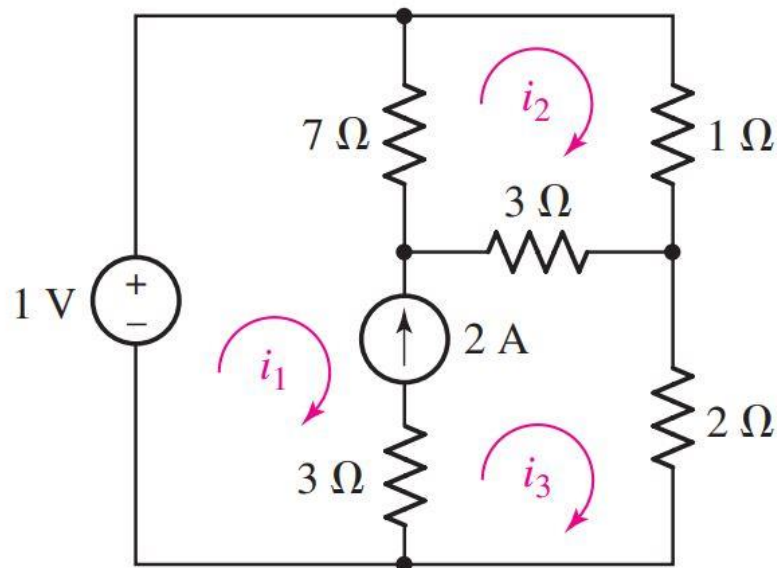
8. Determine the values of three mesh currents in the below circuit:



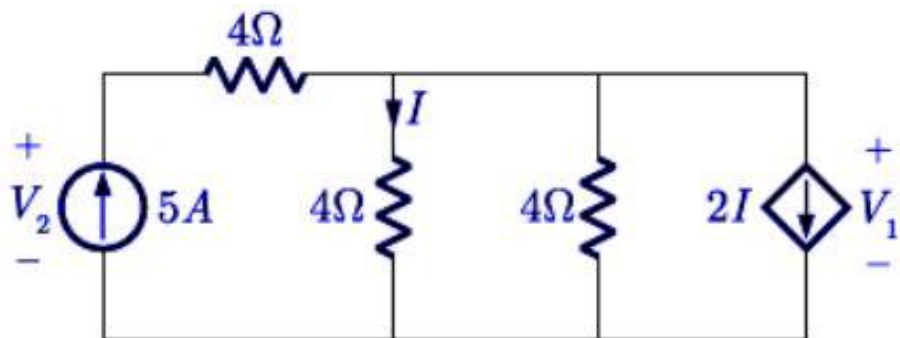
9. In the given circuit find the values of  $V_1$ ,  $V_2$  :



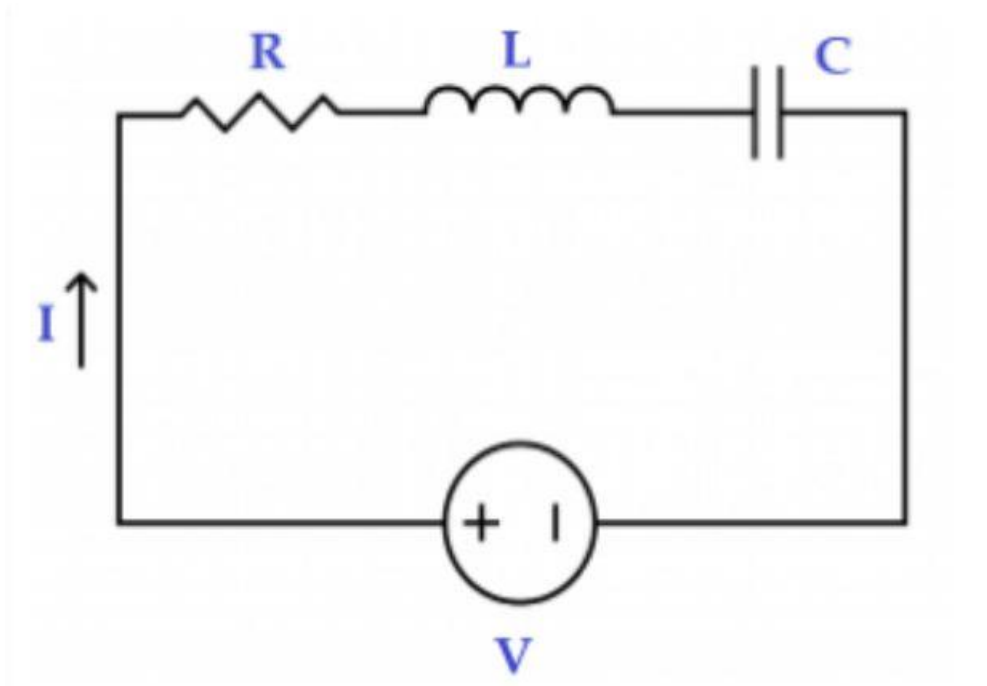
10. Derive the expression of current  $I$  for the given series RLC circuit below:



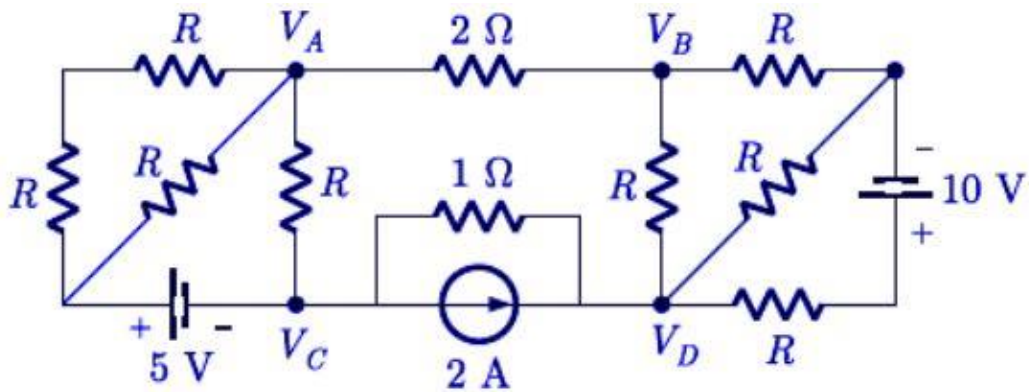
11. If  $V_A - V_B = 6V$ , then find the value of  $V_C - V_D$  in the below circuit:



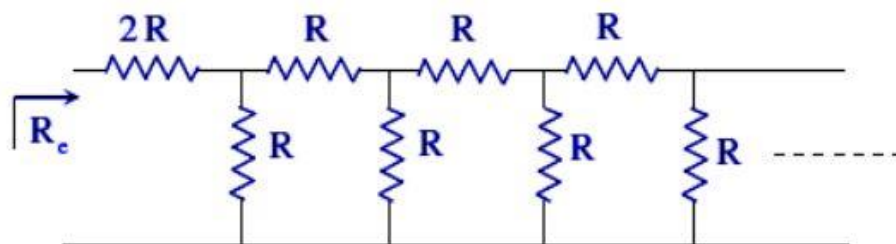
12. The equivalent resistance of infinite ladder shown in below figure is  $R_e$ , then find the value of  $R_e/R$ :



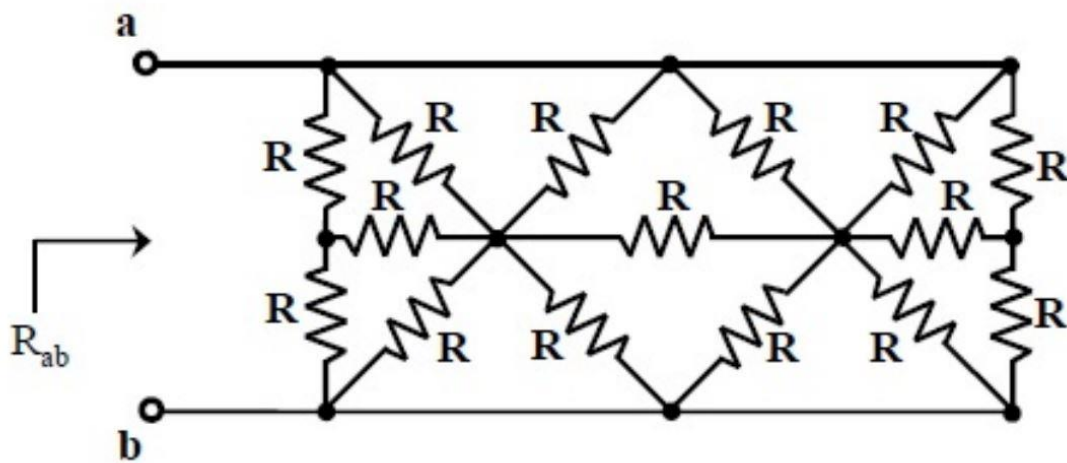
13. In the network shown below, all the resistors are identical with  $R = 300\ \Omega$ , find the equivalent resistance  $R_{ab}$ :



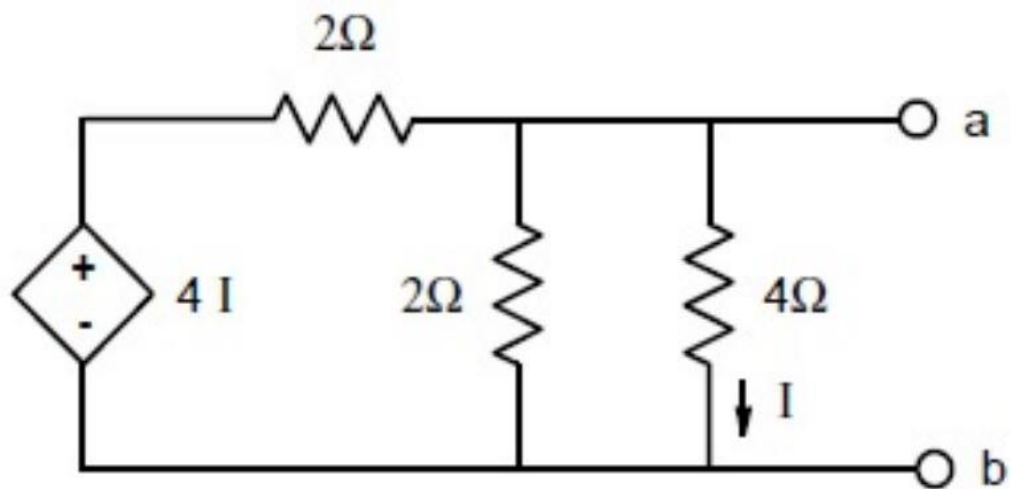
14. In the circuit below, the equivalent resistance between the terminals a and b is:



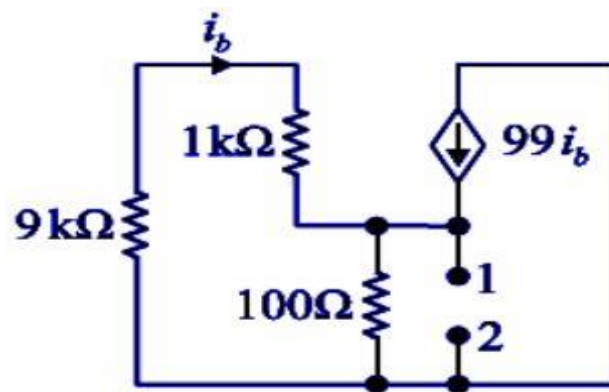
15. Find the equivalent resistance between nodes 1 and 2:



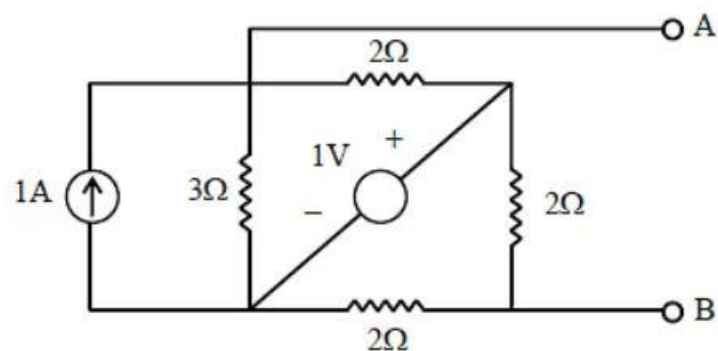
16. The Thevenin impedance across terminal A and B is:



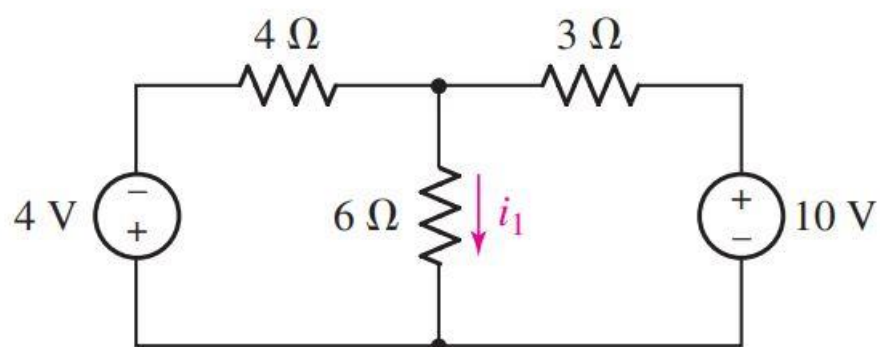
17. Determine the value of current  $i_1$  using superposition theorem and also verify the same using Thevenin's or Norton's theorems treating  $6\Omega$  as the load resistance:



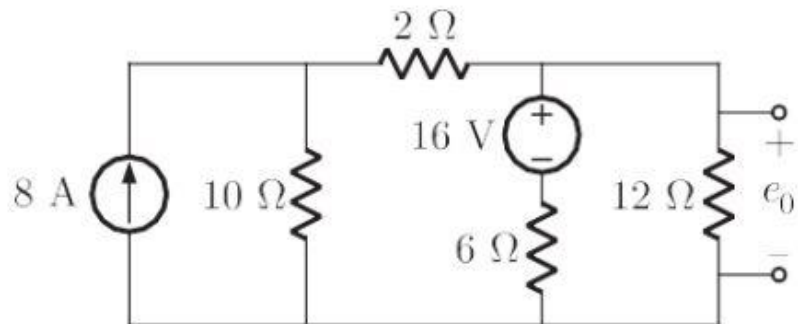
18. Find value of voltage  $e_0$  using both Thevenin's and Norton's theorems treating  $12\Omega$  as the load resistance:



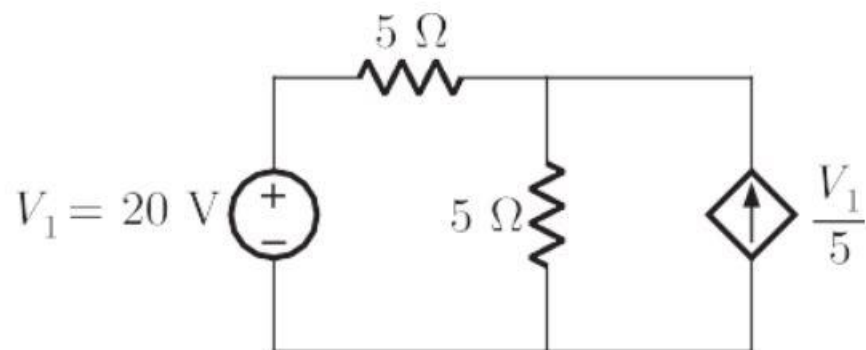
19. Determine the power delivered or absorbed by the dependent current source in the below network:



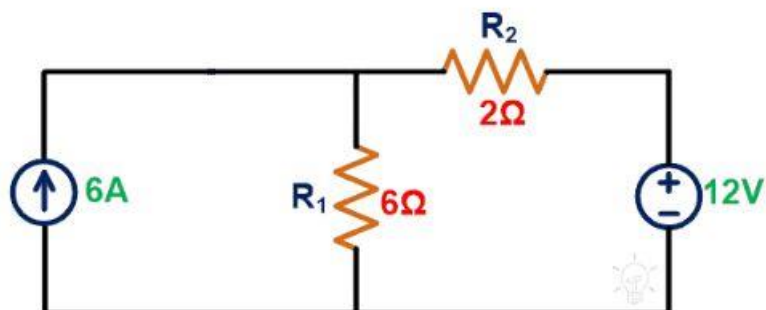20. Find the voltage across  $6A$  current source using Tellegen's theorem:



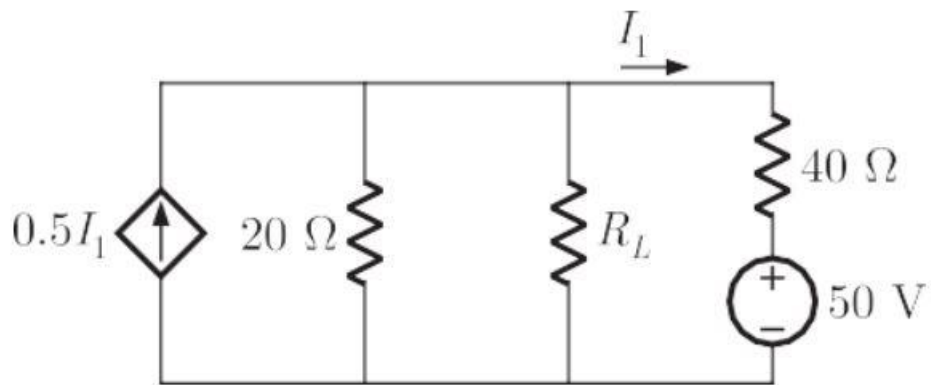21. In the network shown below, the maximum power is delivered to  $R_L$  if its value is:



Answers:

1. 1,2A
2. 1,-4,0A
3. Proof
4. -13,-13/7,5,5/8
5. -1V
6. -8.6,-3.6,-7.6V
7. 2.7272,1.2727A
8. -1.21875,-0.5625,0.78125A
9. 5V,25V
10. -5V
11. proof
12. 2.618
13. 100
14. 4/3
15. 50
16. 11/5
17. 14/27A
18. 28V
19. 80W delivered
20. 18V
21. 16W