

## MOSFET TUTORIAL - 1

7. 6.  $g_m = \frac{\partial I_D}{\partial V_{GS}}$

$$I_D = \mu_n C_{ox} \left(\frac{W}{L}\right) \left[ (V_{GS} - V_{th}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\Rightarrow \boxed{\frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left(\frac{W}{L}\right) V_{DS} = g_m}$$

$g_m = 0$  when  $V_{DS} = 0$  because when  $V_{DS} = 0$ , even though channel is present, current will not flow.

Hence, resistance  $= \infty \Rightarrow g_m = \frac{1}{\text{Resistance}} = 0$ .

8.  $R_{ON} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{th})}$

Case-1:  $500 = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) (1 - V_{th})}$  — (1)

Case-2:  $400 = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) (1.5 - V_{th})}$  — (2)

Dividing (1) by (2),  $\frac{5}{4} = \frac{1.5 - V_{th}}{1 - V_{th}}$

$$\Rightarrow 5 - 5V_{th} = 6 - 4V_{th}$$

$$\Rightarrow V_{th} = -1V, \text{ which is not possible}$$

as  $V_{th}$  cannot be negative.

$$7. \mu_n C_{ox} = 200 \mu A/V^2$$

$$R_{ON} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs} - V_{th})}$$

$$= \frac{1}{200 \times 10^{-6} \times 20 (1.8 - V_{th})}$$

$$= \frac{250}{1.8 - V_{th}}$$

For minimum  $R_{ON}$ ,  $V_{th} \approx 0$

$$\Rightarrow \text{Minimum } R_{ON} = \frac{250}{1.8} = 138.88 \Omega$$

## TUTORIAL - 2

$$1. V_{DS} = V_{DD} - R_D I_D = V_{DD} - R_D \mu_n C_{ox} \left(\frac{W}{L}\right) \left[ (V_{gs} - V_{th}) V_{ds} - \frac{1}{2} V_{ds}^2 \right]$$

$$\Rightarrow 1 = V_{DD} - R_D (\mu_n C_{ox}) \left(\frac{W}{L}\right) \left[ (V_{gs} - V_{th}) - \frac{1}{2} V_{ds} \right]$$

$$\Rightarrow V_{ds} = \frac{V_{DD} - 1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D}$$

$$V_{ds} = (V_{gs} - V_{th}) - \frac{V_{DD} - 1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D}$$

$$\Rightarrow V_{ds} = (1 - 0.4) - \frac{0.8}{(10^{-4}) \left(\frac{2}{0.18}\right) (10^3 \times 5)}$$

$$= 0.6 - \frac{0.072}{5 \times 10^{-1}} = 0.6 - \frac{0.72}{5}$$

$$= \frac{2.28}{5} = 0.456 V$$



$$I_D R_D + V_{DS} = V_{DD}$$

$$\Rightarrow I_D \times 5 \times 10^3 = 1.8 - 0.456$$

$$\Rightarrow \boxed{I_D = 268.8 \mu A}$$

③ At saturation,

$$V_{GS} - V_{th} = V_{DS} = V_{DD} - I_D R_D$$

$$\Rightarrow V_{GS} - V_{th} = V_{DD} - R_D \left[ \mu_n C_{ox} \frac{W}{L} \frac{(V_{GS} - V_{th})^2}{2} \right]$$

Let  $V_{GS} - V_{th} = x$

$$\Rightarrow x = V_{DD} - R_D \mu_n C_{ox} \frac{W}{2L} x^2$$

$$\Rightarrow \left( R_D \mu_n C_{ox} \frac{W}{2L} \right) x^2 + x - V_{DD} = 0$$

$$\Rightarrow x = \frac{-1 + \sqrt{1 + 4V_{DD} \times R_D \mu_n C_{ox} \frac{W}{2L}}}{R_D \mu_n C_{ox} \frac{W}{L}}$$

$$\Rightarrow V_{GS} - V_{th} = \frac{-1 + \sqrt{1 + 2R_D V_{DD} \mu_n C_{ox} \frac{W}{L}}}{R_D \mu_n C_{ox} \frac{W}{L}}$$

$$\Rightarrow \boxed{V_{GS} = \frac{-1 + \sqrt{1 + 2R_D V_{DD} \mu_n C_{ox} \frac{W}{L}}}{R_D \mu_n C_{ox} \frac{W}{L}} + V_{th}}$$

\* To check if it is in saturation region,  $I_D = I_{sat}$   
 Then calculate  $V_{ds}$  from  $V_{DD} - I_D R_D$ , it should be  $\geq V_{gs} - V_{th}$

2. (i) For saturation,  $V_{DS} = V_{GS} - V_{th}$ .

$$V_{GS} - V_{th} = V_{DD} - I_{sat} R_D$$

$$\Rightarrow V_{GS} - V_{th} = V_{DD} - R_D \times \mu_n C_{ox} \left(\frac{W}{L}\right) \frac{(V_{GS} - V_{th})^2}{2}$$

$$\Rightarrow 0.6 = 1.8 - (5 \times 10^3) \times (10^{-4}) \left(\frac{W}{L}\right) \left(\frac{0.36}{2}\right)$$

$$\Rightarrow 0.6 = 1.8 - (0.09) \frac{W}{L}$$

$$\Rightarrow \frac{9}{100} \frac{W}{L} = 1.2$$

$$\Rightarrow \boxed{\frac{W}{L} = \frac{40}{3} = \frac{2.4}{0.18}}$$

For saturation,  $V_{DS} \geq V_{GS} - V_{th}$

For linear,  $V_{DS} < V_{GS} - V_{th}$

(ii)  ~~$V_{DS} = V_{DD} - \frac{V_{DS1}}{R_D}$~~

$$V_{DD} - V_{DS1} = I_D R_D$$

$$1.8 - V_{DS1} = \frac{1}{2} \times 2 \times 10^{-4} \times \frac{40}{3} (0.36) \times 5 \times 10^3$$

$$1.8 - V_{DS1} = 4.8 \times 10^{-4} \times 5 \times 10^3 = 2.4$$

$$V_{DS1} = 1.4 \text{ V } 0.6 \text{ V}$$

$$1.8 - V_{DS2} = \frac{1}{2} \times 2 \times 10^{-4} \times \frac{40}{3} \times 0.36 \times 5 \times 10^3$$




## Multiplexer


Inverting multiplexer :-

A	B	S	out	
		0	$\bar{A}$	$\Rightarrow \bar{S} \cdot \bar{A}$
		1	$\bar{B}$	$\Rightarrow S \cdot \bar{B}$

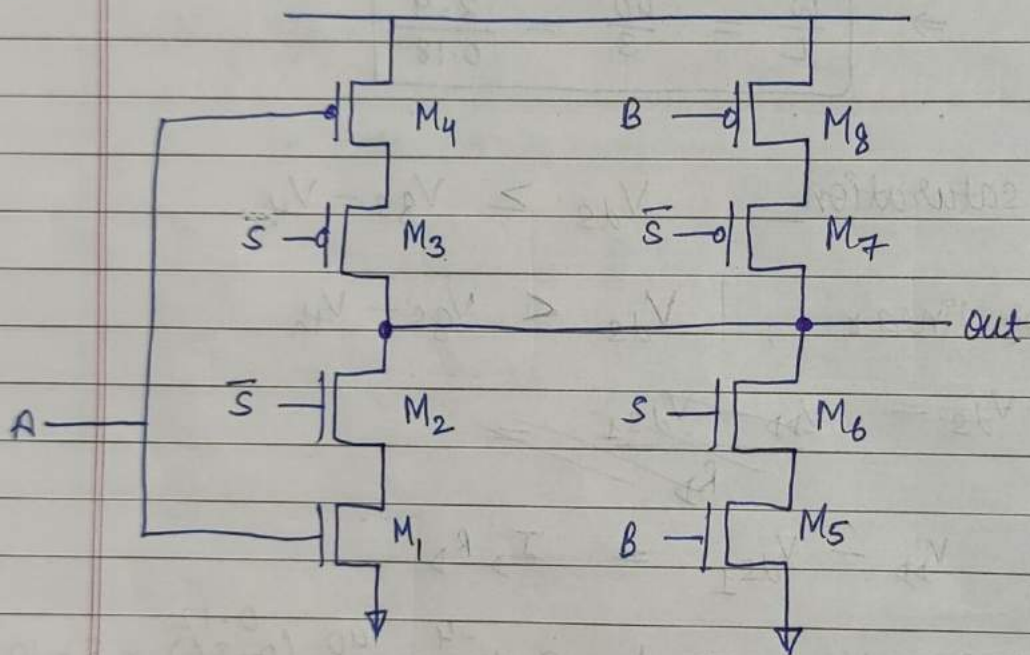
We can invert the result obtained to get multiplexer




When  $S = 0 \Rightarrow \bar{S} = 1$

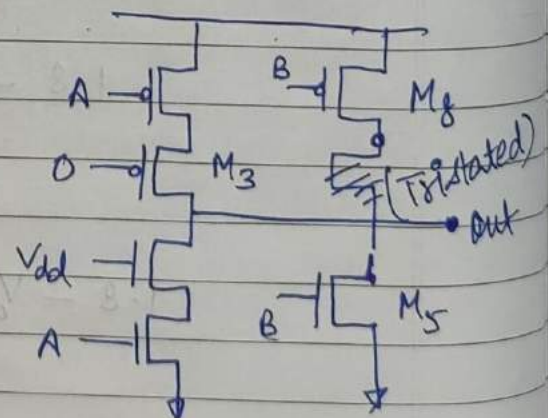
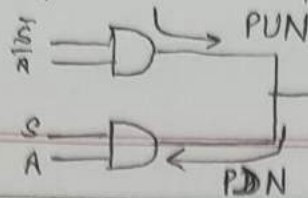
# We cannot do / implement multiplexer using previous created gates as :-



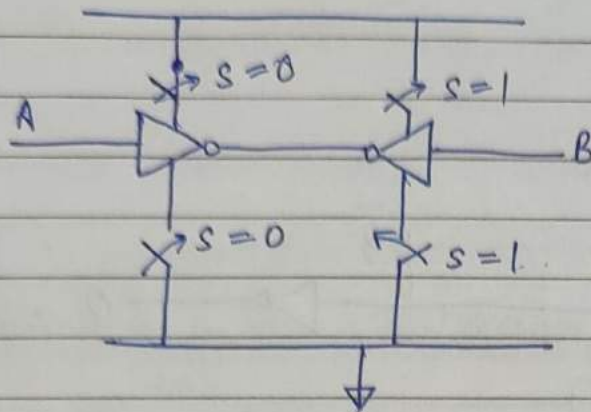
Because PUN will charge  $V_{out}$  & simultaneously PDN will discharge  $V_{out}$



⇒ Logic diagram

(Just idea  
NOT correct  
diagram)


## Latch

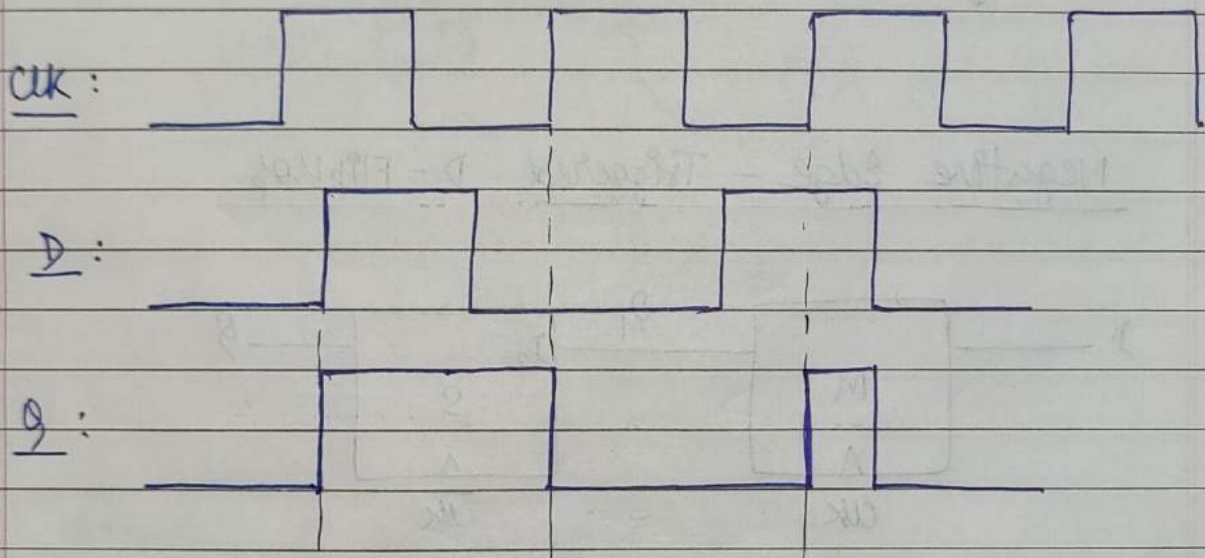



[can realise latch using multiplexer]

Connect clk as selection signal



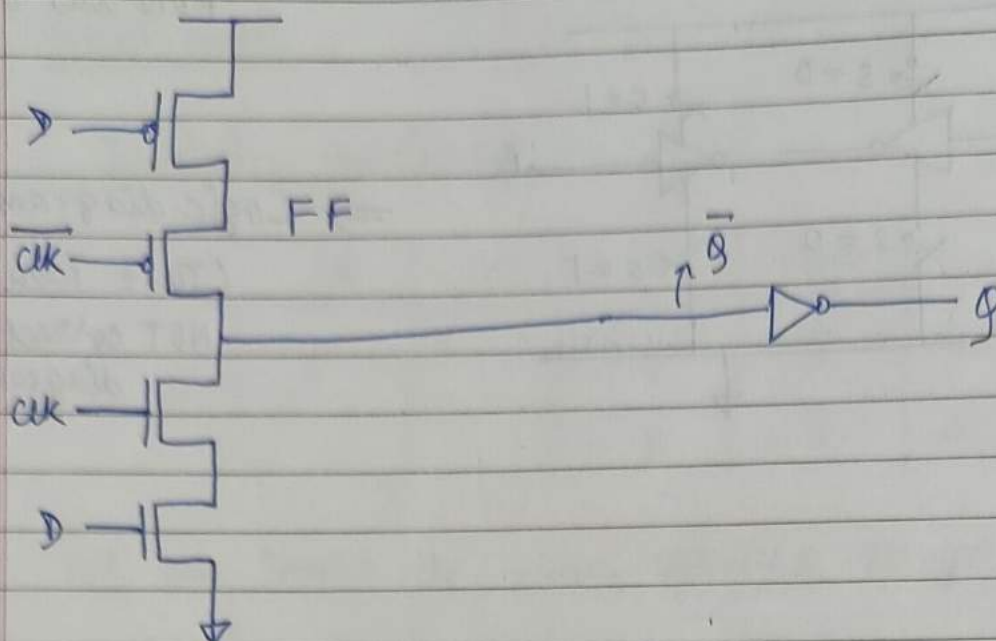

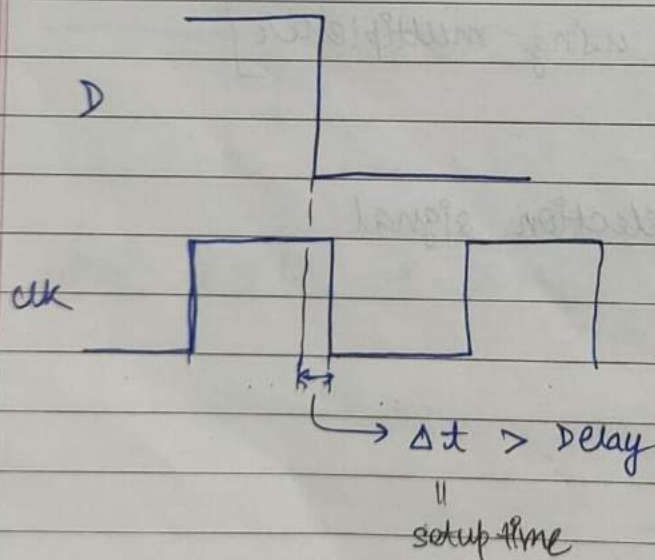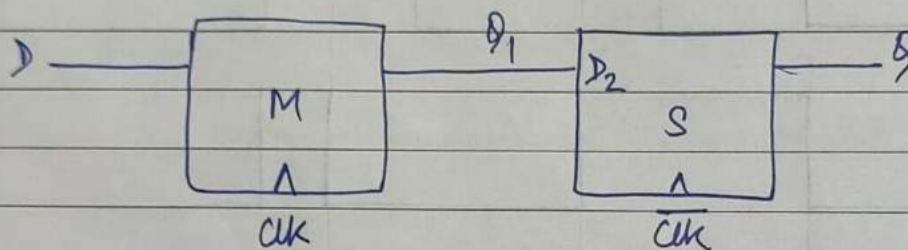
### Negative Edge - Triggered D - Flipflop



For safe functioning of logic,


$$(V_{DD} - V_{OH}) \ll (V_{DD} - V_{OL})$$

### MOSFET in Saturation

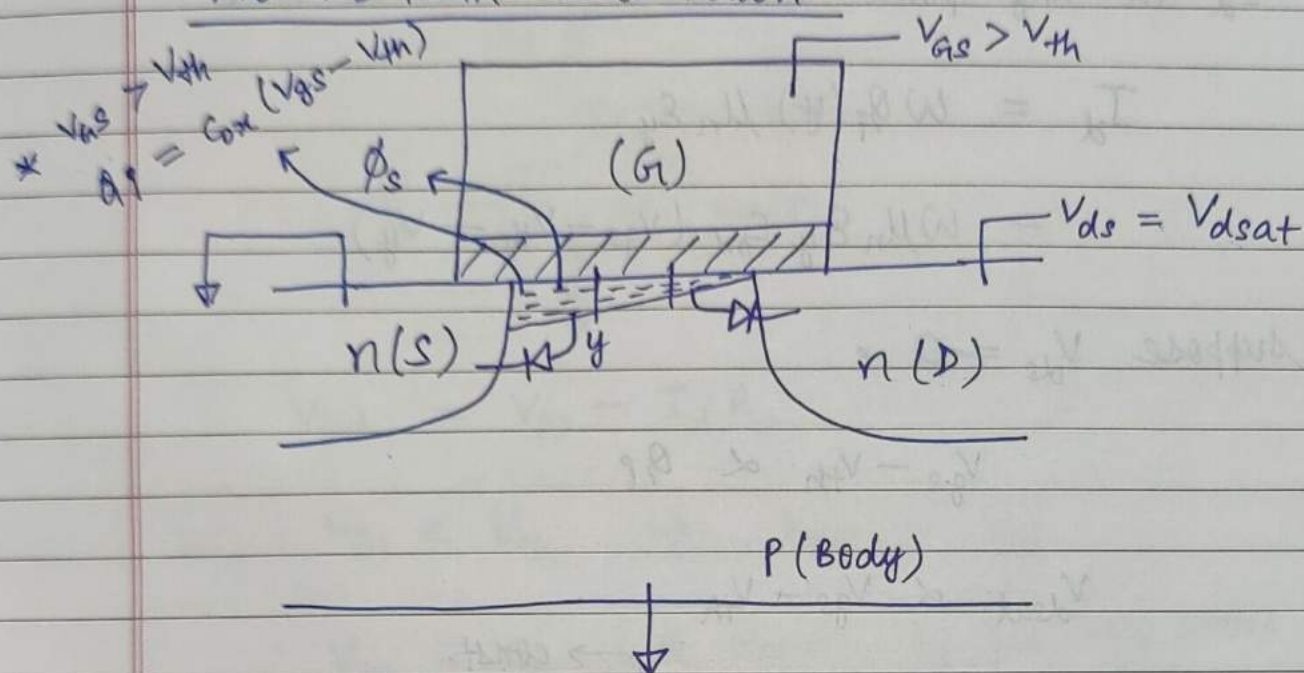

Potential at source edge is  $\phi_s$

Magnified picture :

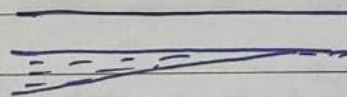

At the drain edge of channel,

$$V_{ds} = 0 \rightarrow \phi_s$$

$$V_{ds} = V_d \rightarrow \phi_s + V_d \quad Q_i (\text{drain edge})$$

$$= C_{ox} [V_{GS} - V_{th} - V_d]$$

$$V_{ds} = V_{dsat} \rightarrow \phi_s + V_{dsat}$$



$$Q_i = 0 = C_{ox} [V_{gs} - V_{th} - V_{dsat}]$$

$$V_{dsat} = V_{gs} - V_{th}$$

$I_d$  at any point in channel should be same.

$$I_d = W Q_i(y) \mu_n E_y$$

$$= W \mu_n E_y C_{ox} (V_{gs} - V_{th} - V_y)$$

Suppose  $V_{ds} = 0$ .

$$V_{gs} - V_{th} \propto Q_i$$

$$V_{dsat} \propto V_{gs} - V_{th}$$

$$E_y = f(V_{dsat}, L) \rightarrow \text{const.}$$

$$\Rightarrow E_y \propto (V_{gs} - V_{th})$$

$$\left[ \begin{aligned} V_{dsat} &= V_{ds} \\ y &= L(D) \\ &= - \int_{y=0(S)}^y E_y dy \\ &= V_{gs} - V_{th} \end{aligned} \right]$$

$$I_d = W \mu_n C_{ox} (V_{gs} - V_{th}) E_y \text{ (source edge)} \rightarrow \propto V_{dsat} = V_{gs} - V_{th}$$


$$I_d \propto V_{ds} (V_{gs} - V_{th})^2$$

$$I_d \propto \frac{W \mu_n C_{ox}}{L} (V_{gs} - V_{th})^2$$

$$\left( E_y \approx \frac{V_{dsat}}{L} = \frac{V_{gs} - V_{th}}{L} \right) \rightarrow$$

## MOS Amplifiers

→ Linearly scaled output

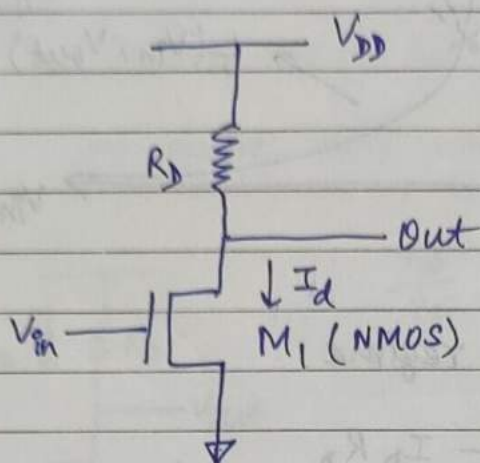

$$V_{out} = V_{DD} - I_d R_D$$

$$V_{in} < V_{th} \Rightarrow V_{out} = V_{DD}$$

$$V_{in} \geq V_{th} \text{ but nearly } V_{th} \left[ \Rightarrow \text{very small current flows} \Rightarrow V_{out} \text{ slightly less than } V_{DD} \right]$$


$$V_{GS} = V_{in} \Rightarrow V_{GS} - V_{th} = V_{dsat} \approx 0$$

$$V_{out} \approx V_{DD} \Rightarrow M_1 \text{ is in saturation}$$

$$I_d = k \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{th})^2$$
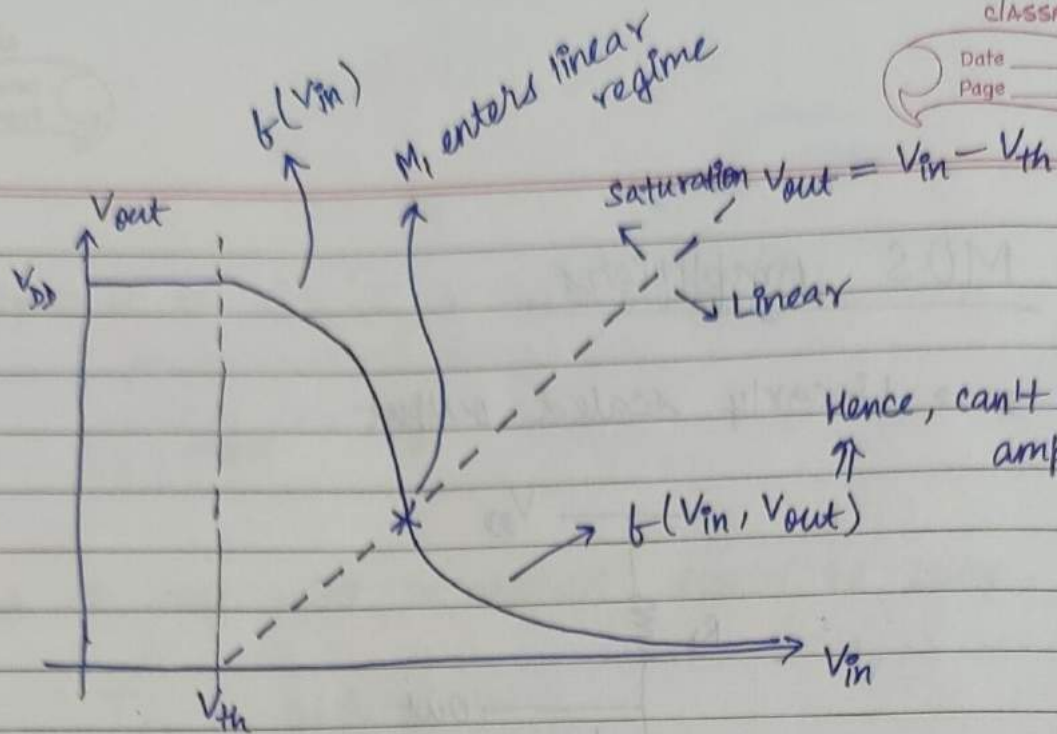
$$V_{out} = V_{DD} - \left[ k \mu_n C_{ox} \left( \frac{W}{L} \right) \underset{\substack{\downarrow \\ V_{in}}}{(V_{GS} - V_{th})^2}} \right] R_D$$





→  $M_1$  enters linear regime

$$V_{out} = V_{DD} - I_D R_D$$

$$= V_{DD} - \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{gs} - V_{th}) R_D$$


$$V_{out} = \frac{V_{DD}}{1 + \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{gs} - V_{th}) R_D}$$

Deep in linear regime

$$I_D = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{gs} - V_{th}) \frac{V_{ds}}{R_D}$$

$$V_{ds} = I_D \times R_M \Rightarrow R_M = \frac{V_{ds}}{I_D} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})}$$

↓  
Resistance dependent on  $V_{gs}$


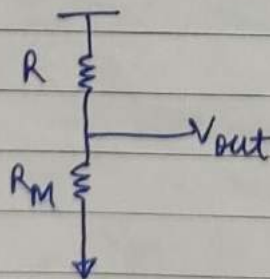


$$V_{out} = \left( \frac{R_M}{R_D + R_M} \right) V_{DD} = V_{DD} \frac{(R_M/R_D)}{(1 + R_M/R_D)}$$

Once it enters linear regime  $I_D$  depends on  $V_{th}$  and  $V_{out}$  both

$\Rightarrow$  We want  $I_D = f(V_{in})$

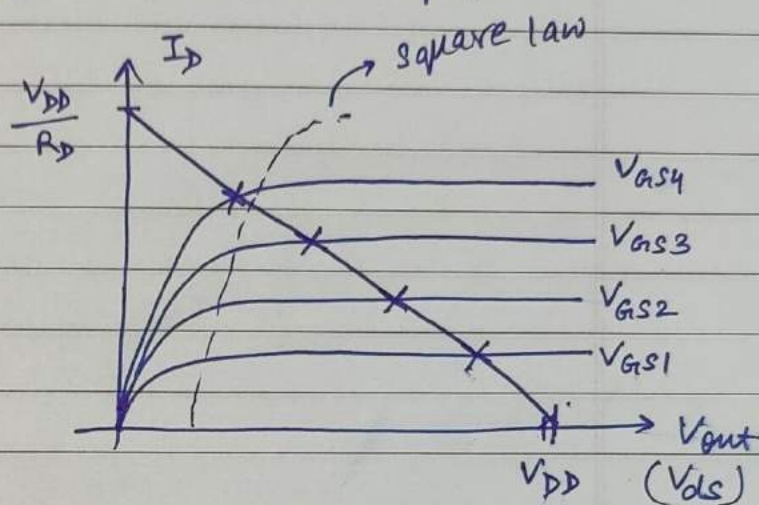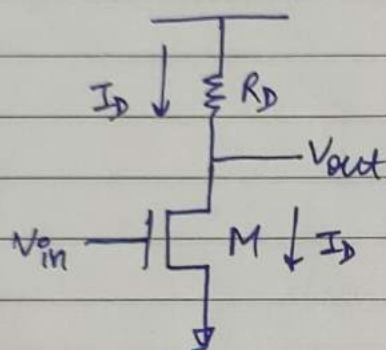$\Rightarrow$  Hence, here can't use as amplifier



$$V_{out} = V_{ds}$$

$$= V_{DD} - I_D R_D = V_{DD} - K_1 (V_{gs} - V_{th})^2 R_D \geq V_{gs} - V_{th} \quad (\text{validity})$$

$$\Rightarrow V_{DD} - K_1 (V_{gs} - V_{th})^2 R_D - V_{out} = 0$$

$$\text{Also, } V_{out} = V_{DD} - I_D R_D$$