

a) Determine the bias current of M_1 , shown in the figure above.

Given :-

$$V_{th} = 0.5V$$

$$\mu_n C_{ox} = 100 \mu A/V^2$$


$$W/L = 5/0.18$$

b) What is the maximum allowable value of R_D for M_1 to remain in saturation.


c) Assume M_1 is in saturation and $R_D = 2.5K\Omega$, Now compute

- (i) Maximum allowable value of W/L
- (ii) Maximum allowable value of R_S with $W/L = 5/0.18$.

 2.) Consider a circuit depicted in figure 2.1, where $W/L = 20/0.18$. Assuming the current flowing through R_2 is $1/10^{th}$ of I_{D1} . Calculate the values of R_1 and R_2 so that $I_{D1} = 0.5mA$.



 3.) In the Common-Source stage, $W/L = 30/0.18$.




- (i) What gate voltage yields a drain current of $0.5mA$? (Verify that M_1 operates in saturation)
- (ii) With such a drain bias, Calculate the voltage gain of the stage.
- (iii) Assume, voltage gain of 5 with $W/L \leq 20/0.18$. Determine the required value of R_D , if the power dissipation must not exceed $1mW$.

 4.) For a MOS differential pair with a common mode voltage (V_{cm}) applied as shown in the fig 4.1

Given :-

- $V_{DD} = V_{SS} = 1V$
- $(W/L)_1 = (W/L)_2 = 12.5$
- $\mu_n C_{ox} = 0.4mA/V^2$
- $V_{th} = 0.5V$
- $I_{SS} = 0.2mA$
- $R_D = 10K\Omega$



Assume current source (I_{SS}) requires a minimum voltage of $0.4V$ to operate properly

Calculate :-

- a.) Find V_{GS} for each transistor.
- b.) For $V_{cm} = 0$, find

- (i) V_S
- (ii) I_D
- (iii) V_D

c.) What is the highest permitted value of V_{cm} for which M_1 and M_2 are in saturation?

5.) For the given MOS differential pair, both MOSFET are perfectly matched and following are the device parameters for both MOSFETs

- $V_{DD} = V_{SS} = 5V$
- $V_{th} = 0.5V$
- $\mu_n C_{ox}(W/L) = 4mA/V^2$
- $R_D = 6K\Omega$

Calculate small signal differential gain?

