

# Universal Shift Register

Sparsh Mittal



# Universal shift register

A register capable of shifting in one direction only is a *unidirectional* shift register.

One that can shift in both directions is a *bidirectional* shift register.

If the register has both shifts and parallel-load capabilities, it is referred to as a *universal shift register*

# Universal shift register

The circuit consists of four  $D$  flip-flops and four multiplexers.

The four multiplexers have two common selection inputs  $s_1$  and  $s_0$ .

Input 0 in each multiplexer is selected when  $s_1s_0 = 00$ , input 1 is selected when  $s_1s_0 = 01$ , and so on.


The selection inputs control the mode of operation of the register according to the function entries in this table.

Mode Control		Register Operation
$s_1$	$s_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load
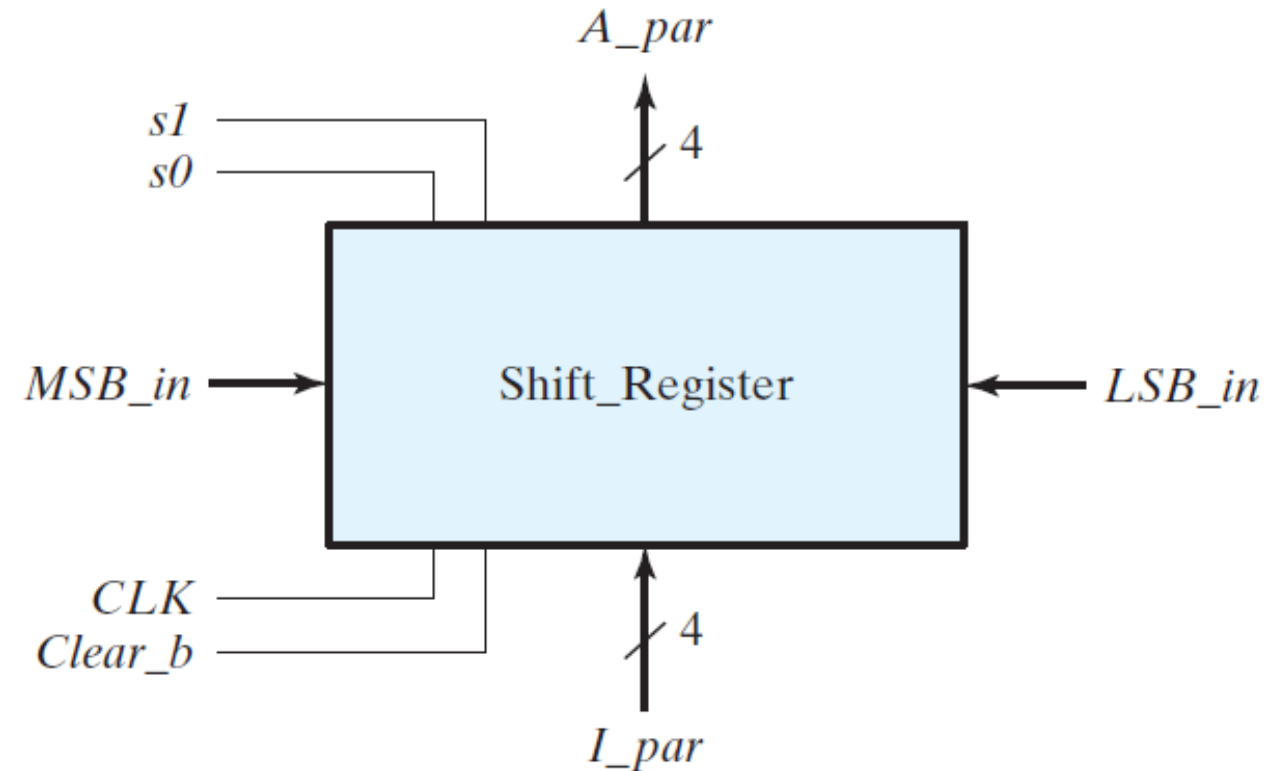
# Overall design


The four multiplexers have two common selection inputs  $s1$  and  $s0$ .

Input 0 in each multiplexer is selected when  $s1s0 = 00$ , input 1 is selected when  $s1s0 = 01$ , and so on.



# Low-level design

Mode Control		
$s_1$	$s_0$	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

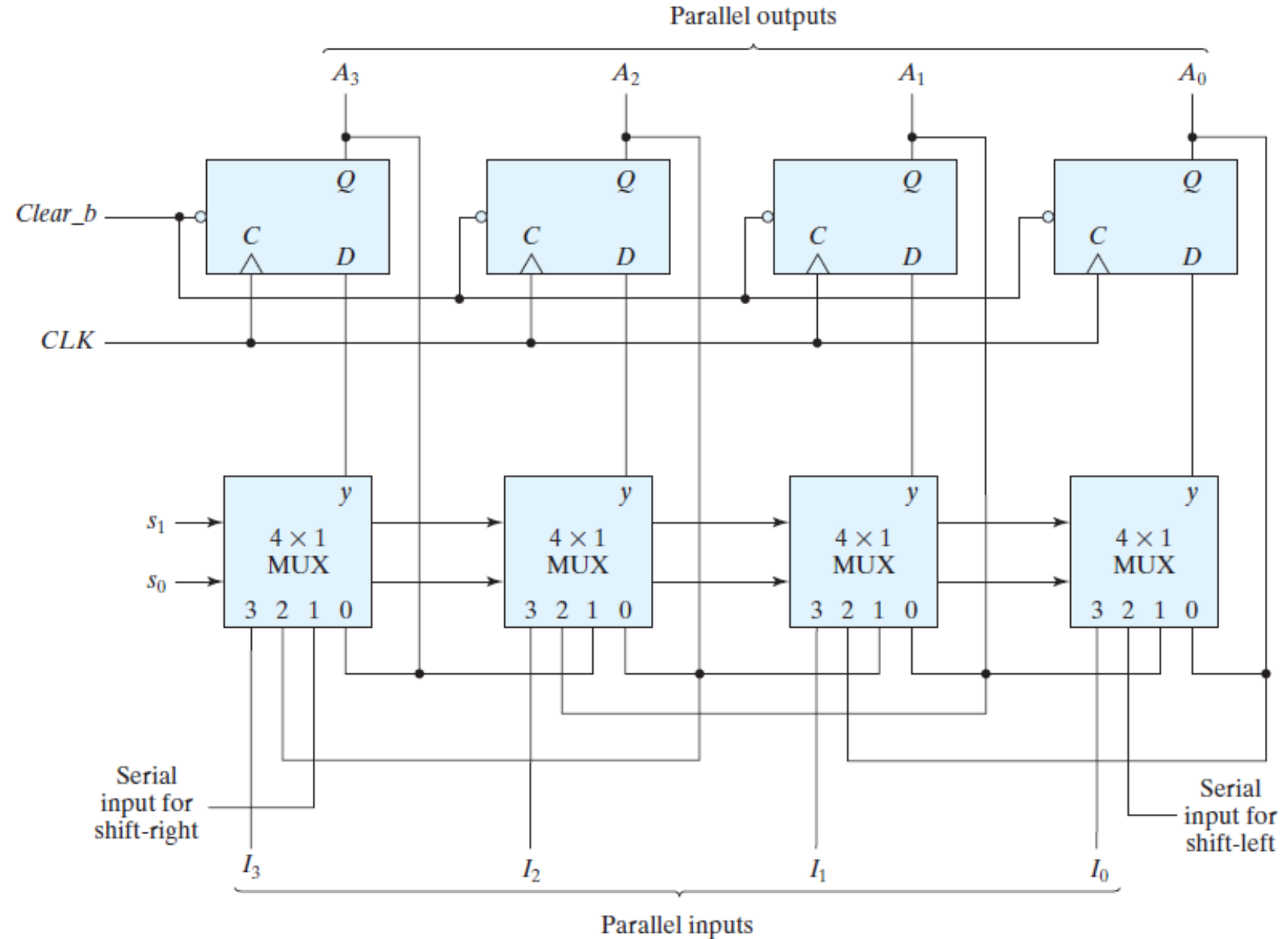

# When $s_1s_0 = 00$

When  $s_1s_0 = 00$ , present value of the register is applied to the  $D$  inputs of the flip-flops.

This condition forms a path from the output of each flip-flop into the input of the same flip-flop, so that the output recirculates to the input in this mode of operation.

The next clock edge transfers into each flip-flop the binary value it held previously, and no change of state occurs.

Mode Control		Register Operation
$s_1$	$s_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

# When $s1s0 = 01$ and $=10$ and $=11$

**When  $s1s0 = 01$ ,** terminal 1 of the multiplexer inputs has a path to the  $D$  inputs of the flip-flops. This causes a shift-right operation, with the serial input transferred into flip-flop  $A3$ .

**When  $s1s0 = 10$ ,** a shift-left operation results, with the other serial input going into flip-flop  $A0$ .



**When  $s1s0 = 11$ ,** the binary information on the parallel input lines is transferred into the register simultaneously during the next clock edge.

Note that data enters  $MSB_{in}$  for a shift-right operation and enters  $LSB_{in}$  for a shift-left operation.
  
# Parallel vs Serial Transfer

To transmit an  $n$  -bit quantity between two far-away points, using  $n$  parallel lines is costly.

It is more economical to use a single line and transmit the information serially.





# Usecase

Shift registers are used to interface digital systems situated remotely.


The transmitter accepts  $n$  -bit data in parallel into a shift register and then transmits the data serially along the common line.

The receiver accepts the data serially into a shift register.

When all  $n$  bits are received, they can be taken from the outputs of the register in parallel.

Thus, the transmitter performs a parallel-to-serial conversion of data and the receiver does a serial-to-parallel conversion.
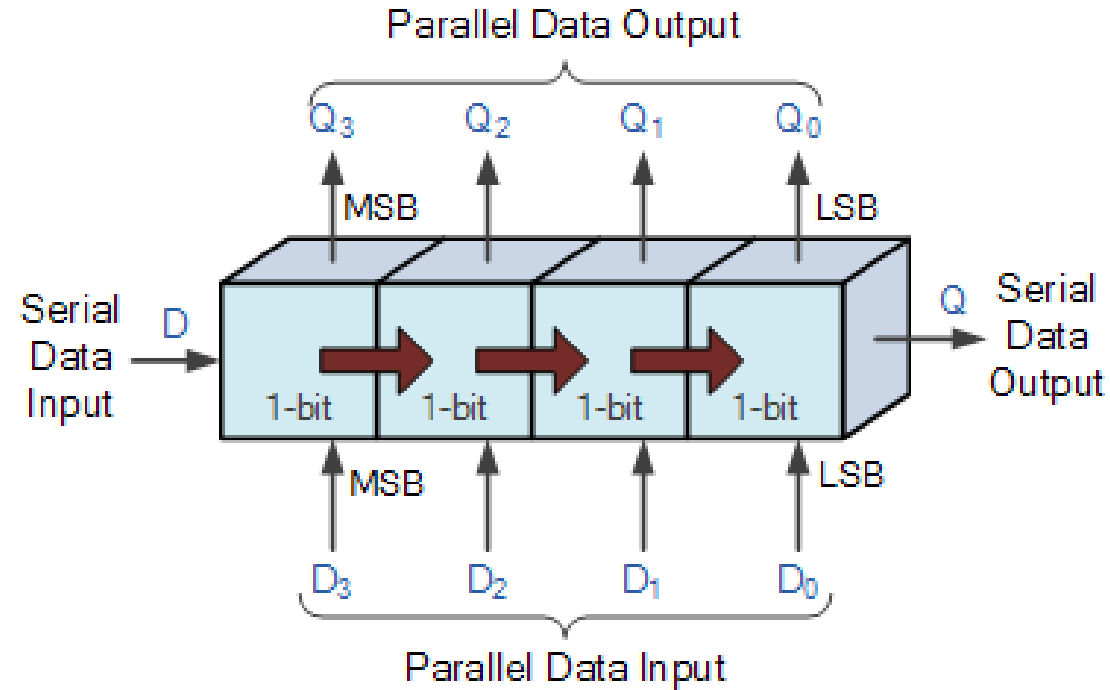
# Shift register for conversion between serial and parallel



# References

[https://www.globalspec.com/learnmore/semiconductors/logic/digital\\_parallel\\_serial\\_converters](https://www.globalspec.com/learnmore/semiconductors/logic/digital_parallel_serial_converters)

[https://www.electronics-tutorials.ws/sequential/seq\\_5.html](https://www.electronics-tutorials.ws/sequential/seq_5.html)