

1. Implement the following functions using multiplexers
  - a.  $F(A, B, C, D) = \sum(3, 4, 9, 11, 15)$
  - b.  $F(x, y, z) = \prod(2, 4, 5, 7)$
2. Construct a J-K flipflop using a D flip-flop
3. Draw the CMOS implementation (Pull-Up Network and Pull-Down Network) for the following functions
  - a.  $F(A, B, C, D) = \sum(3, 4, 9, 11, 15)$
  - b.  $F(x, y, z) = \prod(2, 4, 5, 7)$
  - c. 4 input *AND* gate
  - d. 4 input *OR* gate
4. For a given technology, NMOS and PMOS have on-state (conducting) resistance of  $100\Omega$  and off-state (non-conducting) resistance of  $1M\Omega$ . Calculate the output voltage if the input is (a) 1 and (b) 0. Assume supply voltage is 1V.