

JK and T Flipflop

Sparsh Mittal


Versatility of JK flipflop

A flipflop can do three operations: Set it to 1, reset it to 0, or complement its output.


But, D flipflop can do only two operations since it has only 1 input.

Synchronized by a clock signal, the JK flip-flop has two inputs and performs all three operations.

JK Flip-flop

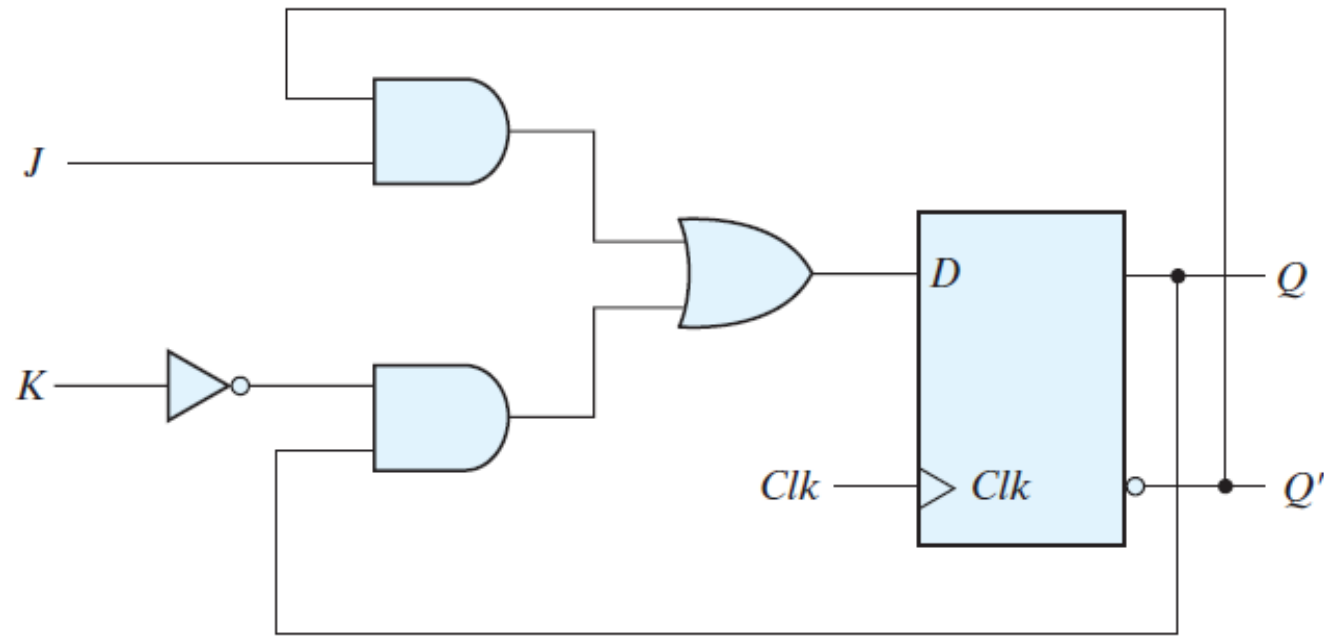

(a) Circuit diagram

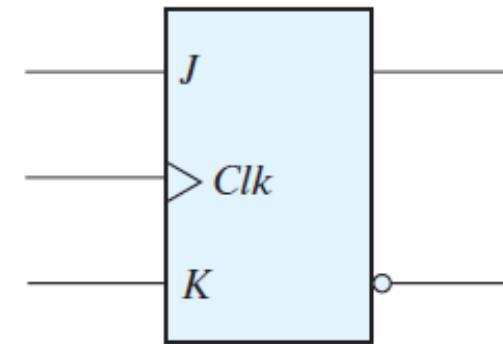

(b) Graphic symbol

FIGURE 5.12
JK flip-flop

JK flipflop

$$D = JQ' + K'Q$$

The J input sets the flip-flop to 1, the K input resets it to 0, and when both inputs are enabled, the output is complemented.

When $J = 1$ and $K = 0$, $D = Q + Q' = 1$, so the next clock edge sets the output to 1.

When $J = 0$ and $K = 1$, $D = 0$, so the next clock edge resets the output to 0.

When both $J = K = 1$ and $D = Q'$, the next clock edge complements the output.

When both $J = K = 0$ and $D = Q$, the clock edge leaves the output unchanged.

Toggle (T) flipflop

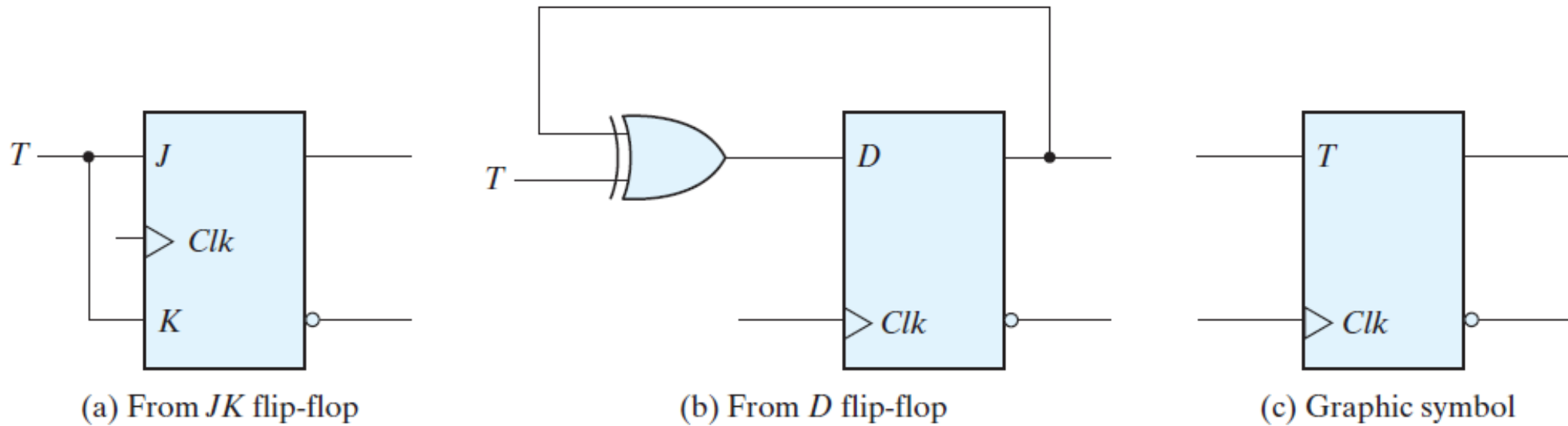


FIGURE 5.13
 T flip-flop

$$D = T \oplus Q = TQ' + T'Q$$

The complementing flip-flop is useful for designing binary counters.

Characteristic table

Table 5.1
Flip-Flop Characteristic Tables

<i>JK Flip-Flop</i>			
<i>J</i>	<i>K</i>	<i>Q(t + 1)</i>	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

<i>D Flip-Flop</i>		
<i>D</i>	<i>Q(t + 1)</i>	
0	0	Reset
1	1	Set

<i>T Flip-Flop</i>		
<i>T</i>	<i>Q(t + 1)</i>	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Characteristic Equation

$$Q(t + 1) = D$$

$$Q(t + 1) = JQ' + K'Q$$

$$Q(t + 1) = T \oplus Q = TQ' + T'Q$$

Asynchronous (direct) set/reset


Some flip-flops have asynchronous inputs to force the flip-flop to a particular state independently of the clock.

Direct set/reset: setting flip-flop to 1 or 0.


When power is turned on, the state of the flip-flops is unknown.

Direct inputs bring all flip-flops to a known starting state prior to the clocked operation.

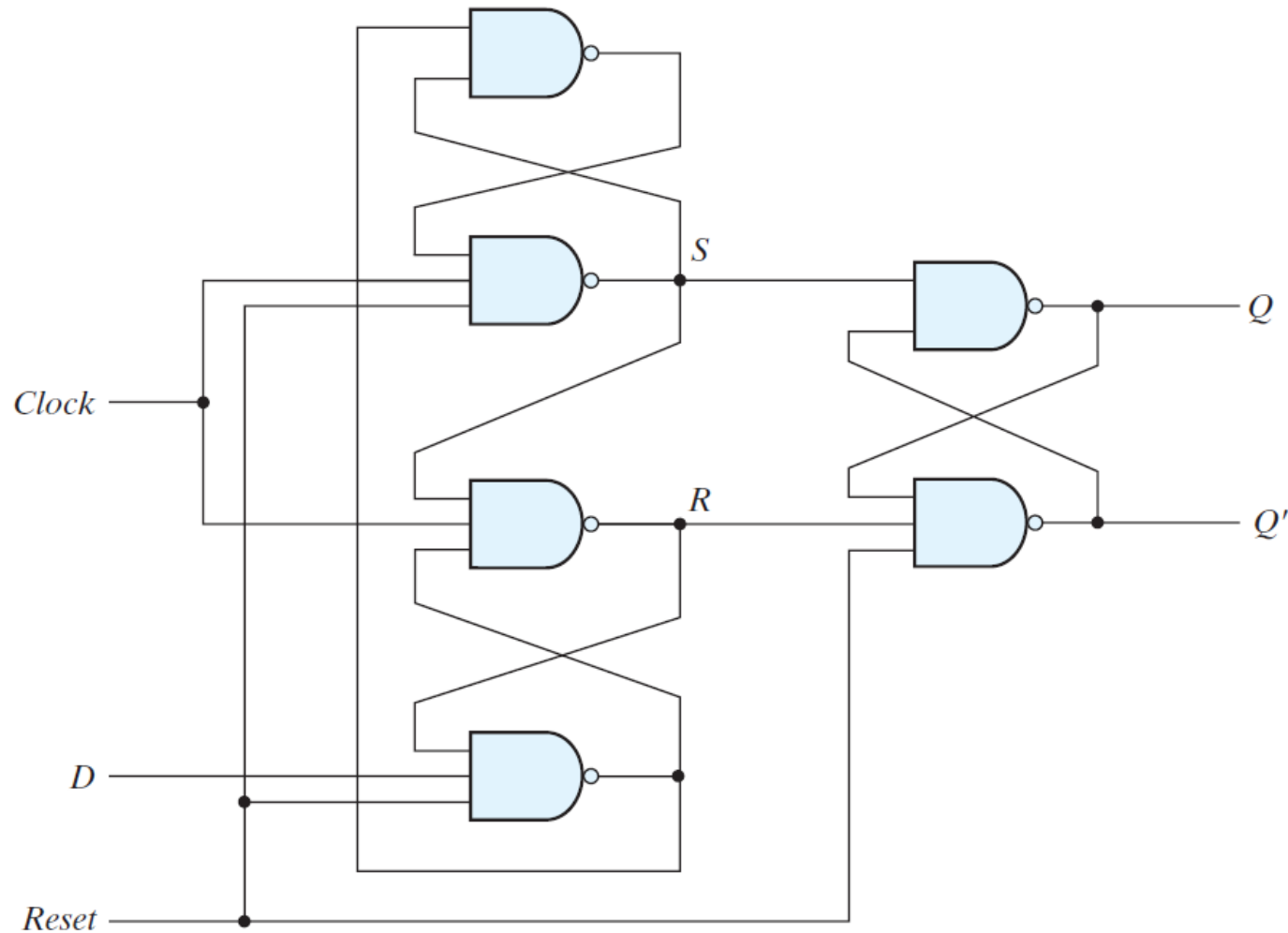Positive-edge-triggered D flip-flop with active-low asynchronous reset



(a) Circuit diagram

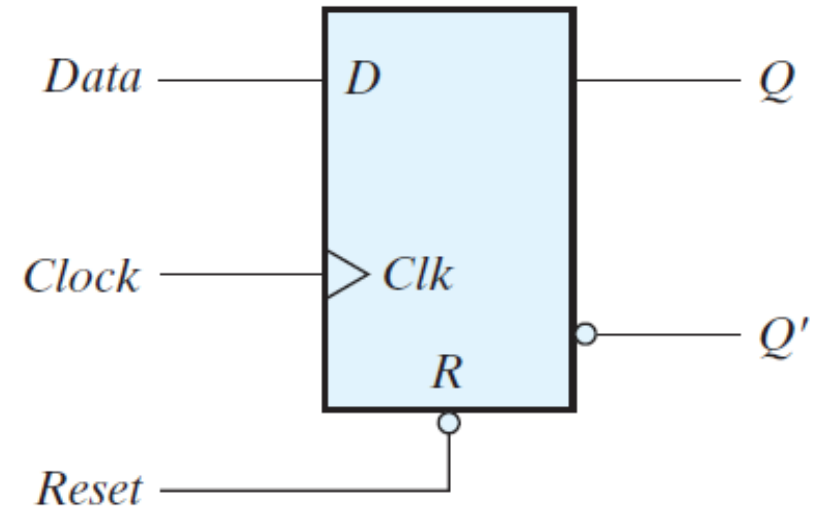

(b) Graphic symbol

R	Clk	D	Q	Q'
0	X	X	0	1
1	\uparrow	0	0	1
1	\uparrow	1	1	0

(b) Function table